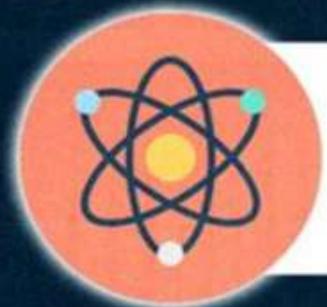




# PARISHRAM



2026


Lecture - 01

## Alternating Current

PHYSICS

Lecture - 1

BY - RAKSHAK SIR

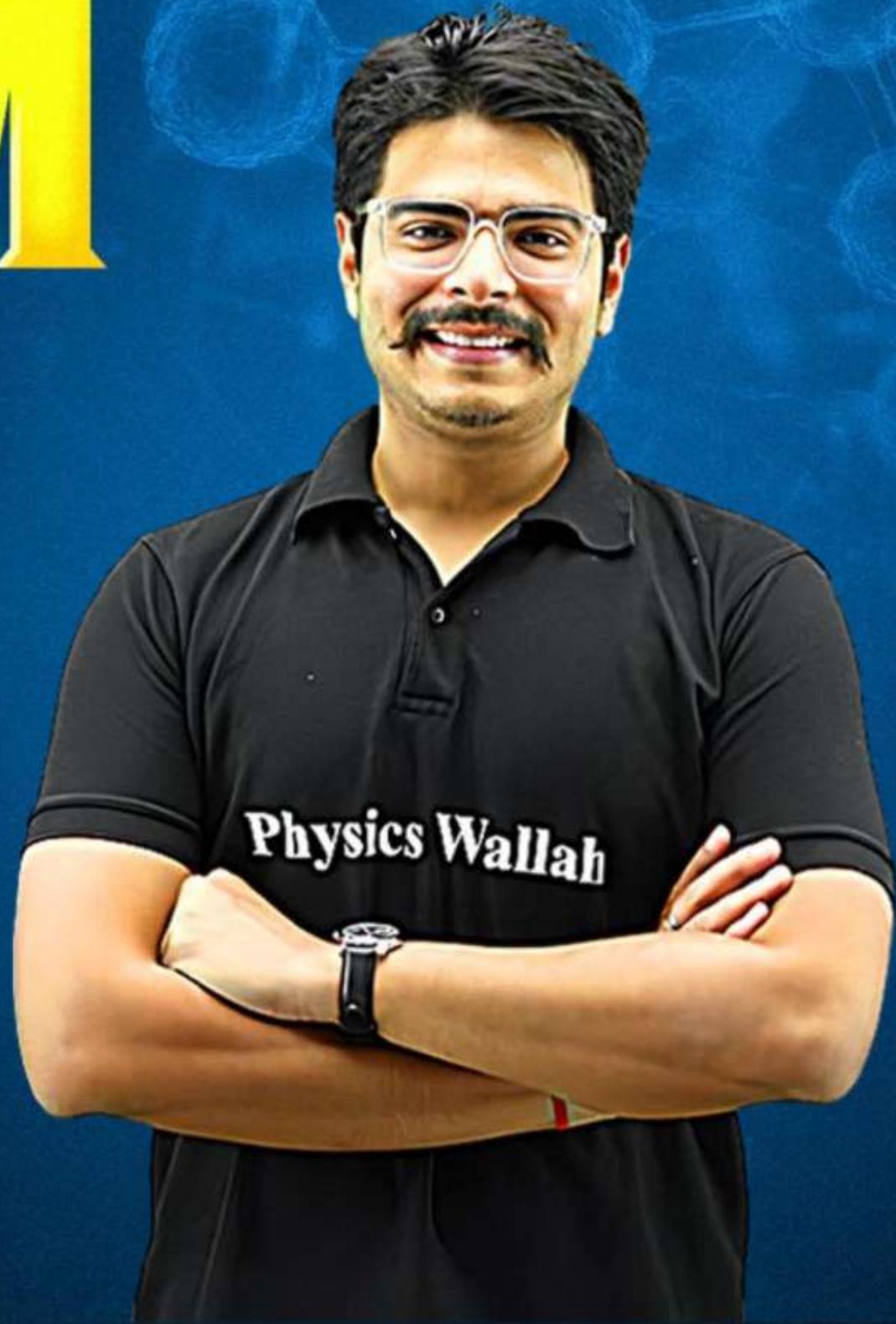

# Topics *to be covered*

- 1 ✓ Average and RMS Value of AC
- 2
- 3

<b>Unit-III</b>	<b>Magnetic Effects of Current and Magnetism</b>	
	<del>✓ Chapter-4: Moving Charges and Magnetism</del>	
	<del>✓ Chapter-5: Magnetism and Matter</del>	
<b>Unit-IV</b>	<b>Electromagnetic Induction and Alternating Currents</b>	
	<del>✓ Chapter-6: Electromagnetic Induction</del>	
	<del>Chapter-7: Alternating Current</del>	<i>'Egn of an SHM'</i>

## Chapter-7: Alternating Current

Alternating currents, peak and RMS value of alternating current/voltage; reactance and impedance; LCR series circuit (phasors only), resonance, power in AC circuits, power factor, wattless current. AC generator, Transformer.

EMI



# Alternating Current (AC)




$$\begin{aligned} \mathcal{E} &= \mathcal{E}_0 \sin \omega t \\ i &= i_0 \sin \omega t \\ i &= \left( \frac{NBA\omega}{R} \right) \sin \omega t \end{aligned}$$

The current which changes its direction after a regular interval of time is called alternating current.



## Feel of AC:


D.C.  $\rightarrow$  Battery

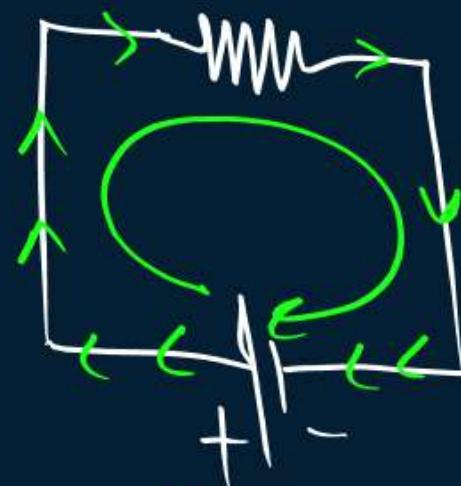

DC Supply




A.C.  $\rightarrow$  A.C. Generator

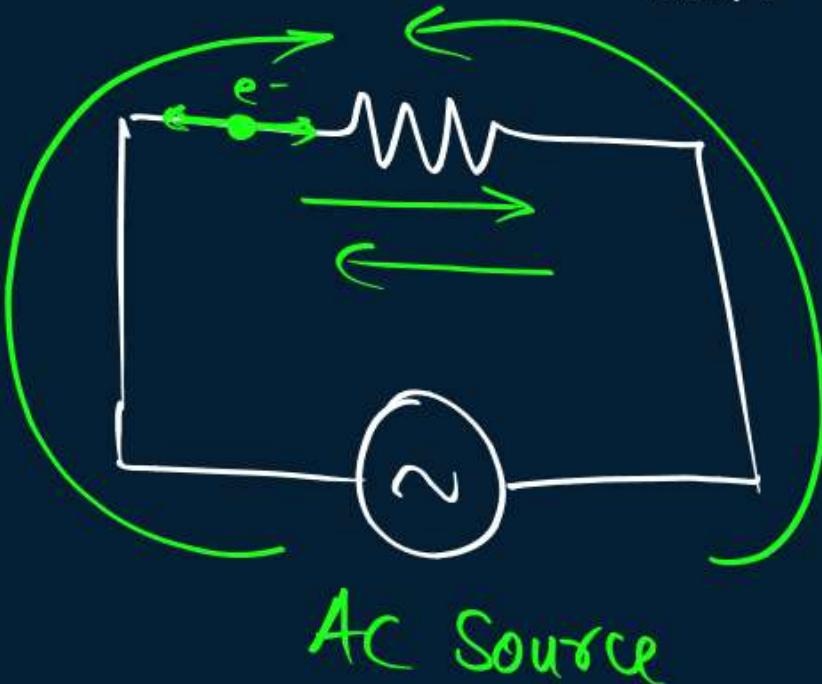




# Types of Alternating Currents

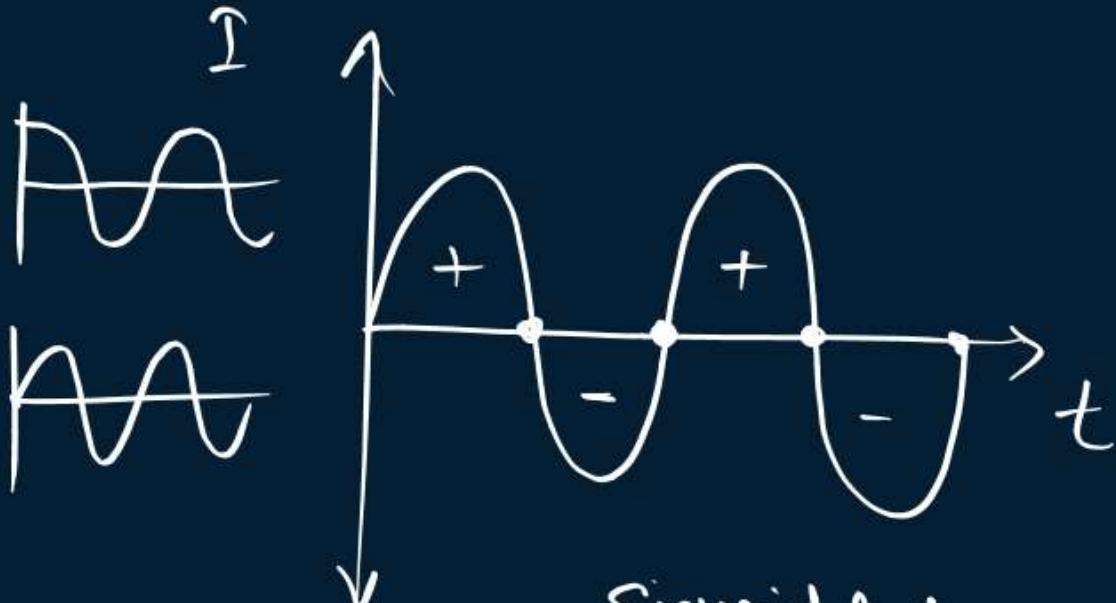


Sinusoidal A.C.

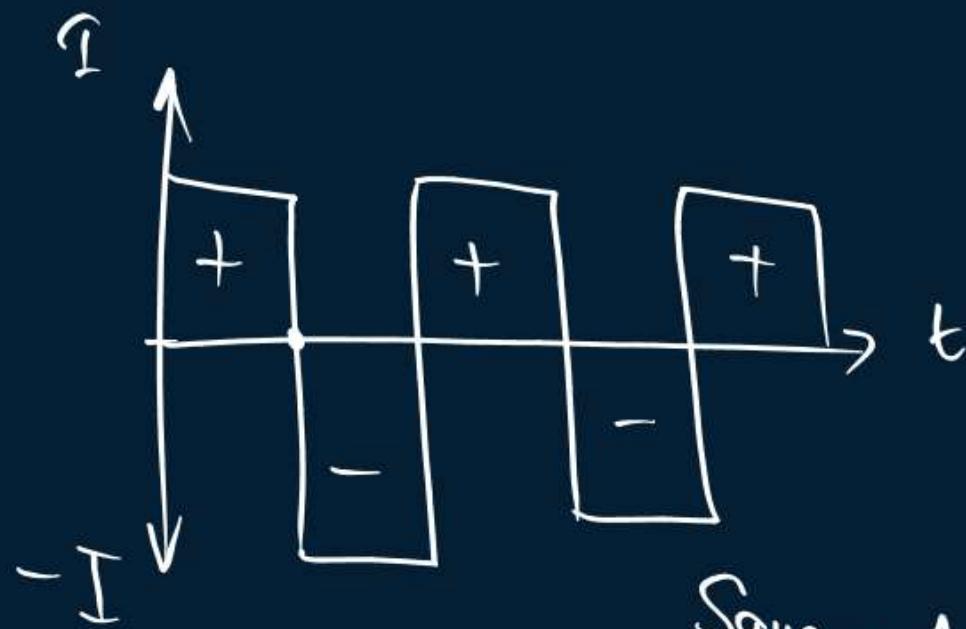


Square A.c.



Saw-tooth A.C.

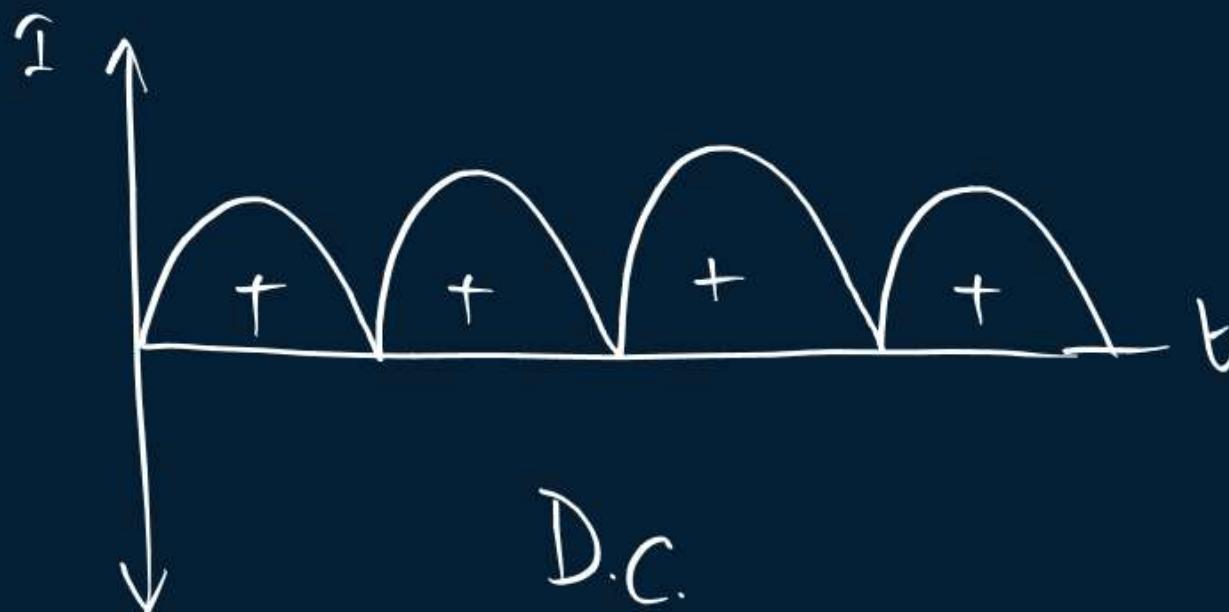

D.C.

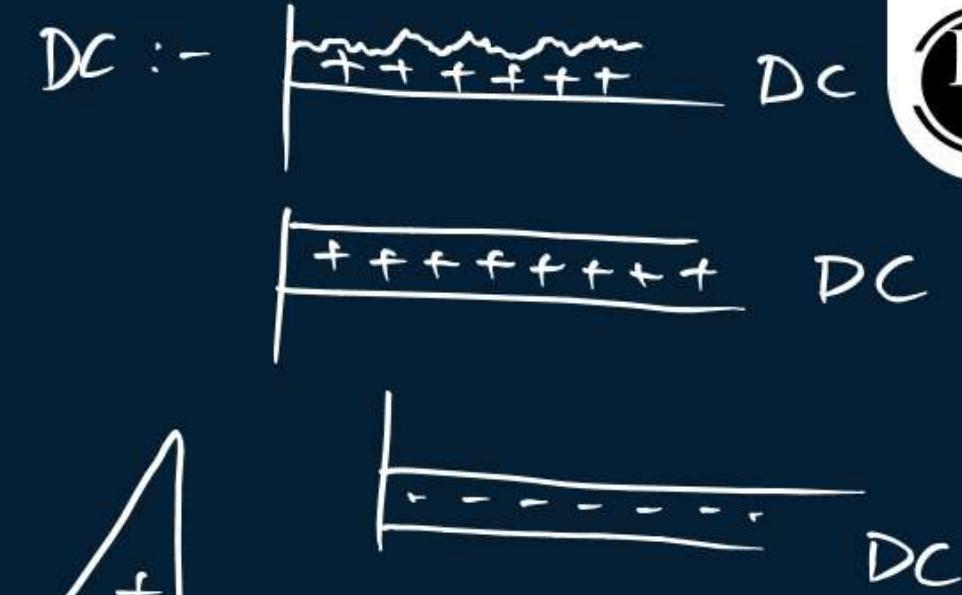



# Home Supply of Alternating Current

$$i = i_0 \sin(\omega t)$$

Alternating current (time varying)      Peak value of A.C. (Current Amplitude)      Angular frequency (rad/sec)      any time 't'

# Angular frequency ( $\omega$ ) :-

$$\omega = \frac{2\pi}{T}$$


$$\omega = 2\pi\nu$$

Angular freq. ←      frequency →

Alternating Voltage       $V_{rms} = 220 \text{ Volts}$  @  $\nu = 50 \text{ Hz}$   
 In U.S.A. =  $110 \text{ V} @ 60 \text{ Hz}$


$$\begin{aligned} \nu &= 50 \text{ Hz} \\ \omega &= 2\pi\nu \\ &= 2\pi 50 \\ &= 100\pi \text{ rad/sec} \end{aligned}$$

$$I = I_0 \sin \omega t$$

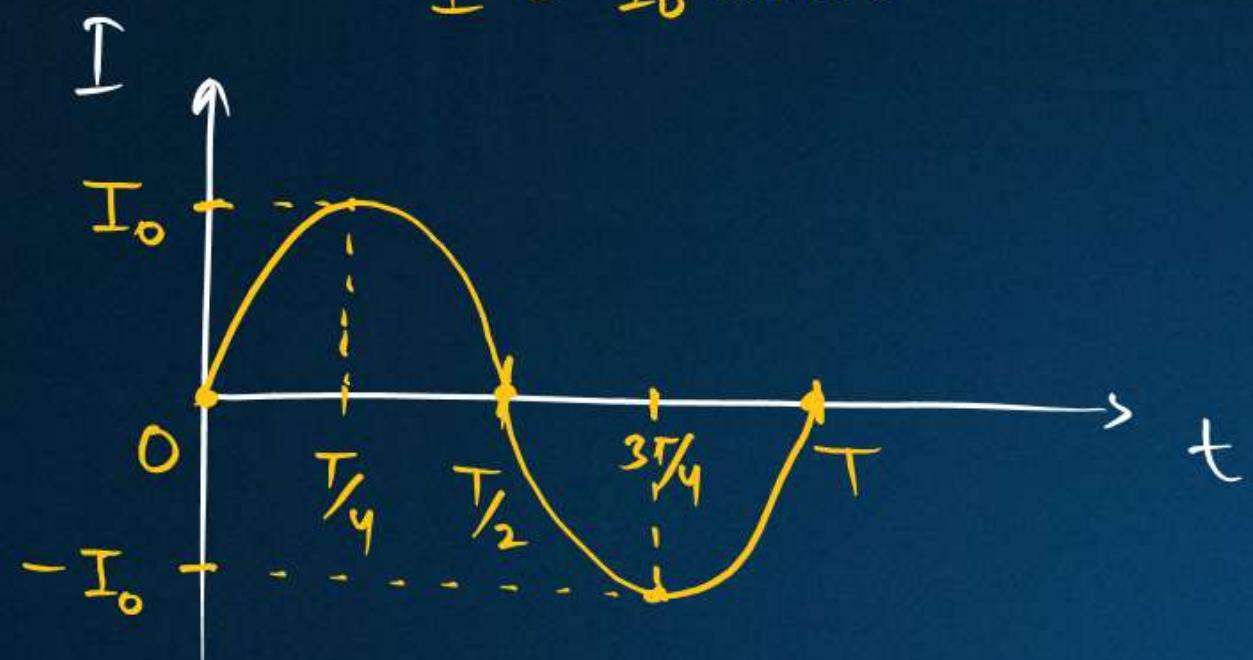

- i) One cycle complete  $\rightarrow$  Time Period ( $T$ )
- ii) half cycle complete  $\rightarrow$   $T/2$

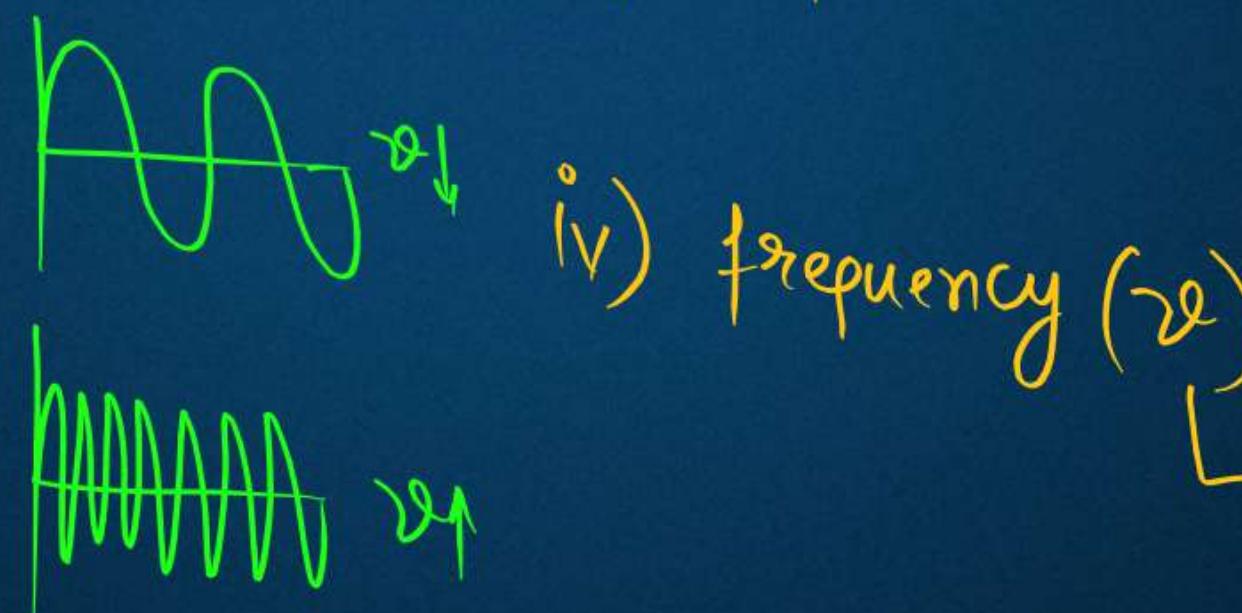iii) Amplitude  $\rightarrow$  Maximum Value ( $I_0$ )



iv) frequency ( $\nu$ )  
 SI unit  $\Rightarrow$  hertz (Hz)

How many times in Indian home supply, the current changes its direction in 1 second?




$$\omega = 50 \text{ Hz}$$

1 sec  $\rightarrow$  50 Baar oscillations

1 oscillation  $\rightarrow$  2 directions
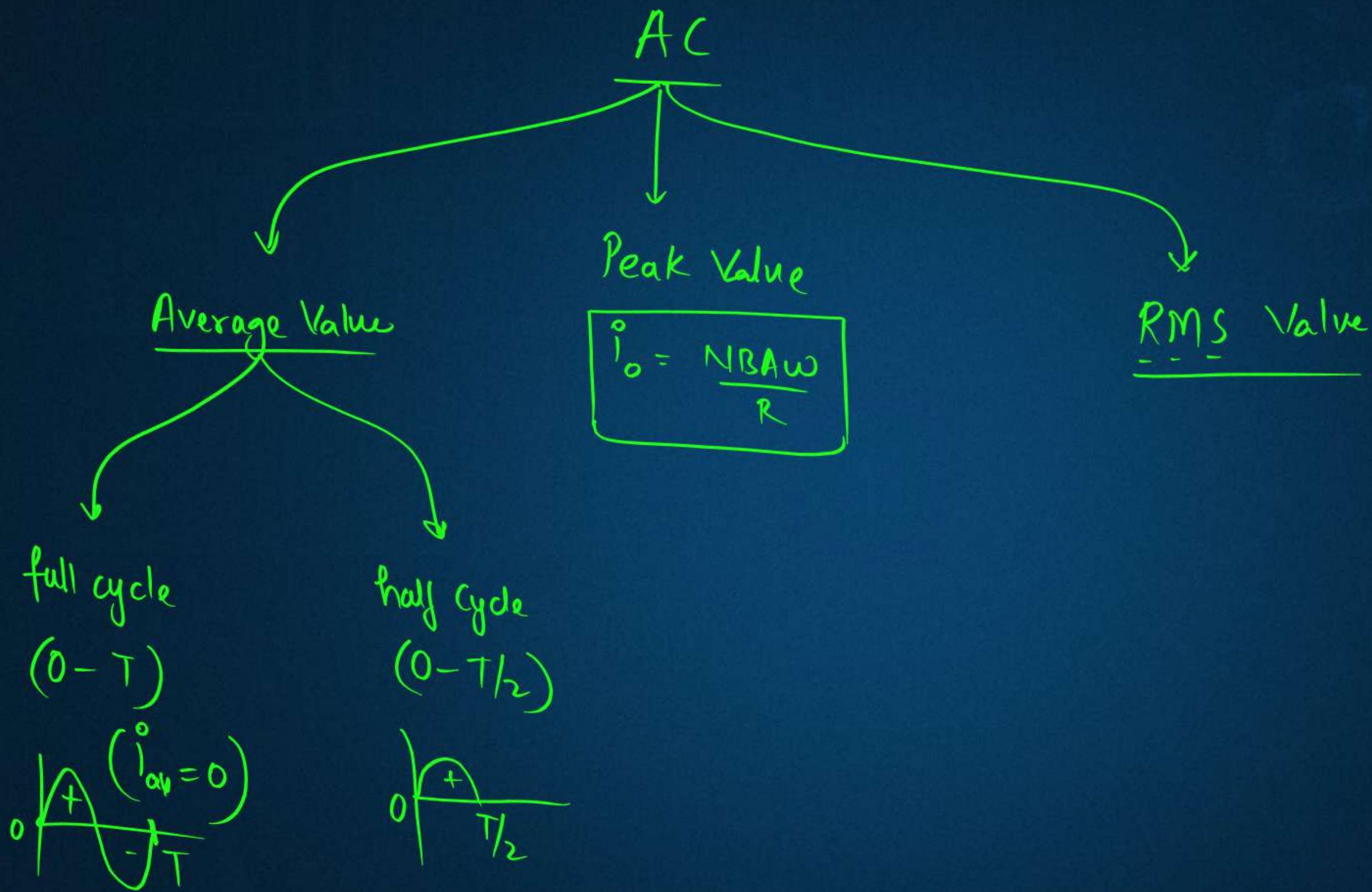
$$50 \longrightarrow 50 \times 2 = 100 \text{ Baar direction change}$$





# Average Current in Sinusoidal AC (RVSN)

It is the constant current which must be flown through equivalent DC circuit, so that same charge flows in both the circuits in a given time.

\* For Full Cycle (0 - T)

$$\dot{q} = \frac{dq}{dt}$$

$$dq = i \cdot dt$$

Int. both sides ...

$$\int dq = \int_0^T i \cdot dt$$



$$\int dq = \int_0^T i_0 \sin \omega t \cdot dt \quad [i = i_0 \sin \omega t]$$

$$q = i_0 \int_0^T \sin \omega t \cdot dt$$

$$q = i_0 \left[ -\frac{\cos \omega t}{\omega} \right]_0^T$$

$$q = \frac{i_0}{\omega} \left[ -\cos \omega t \right]_0^T$$

$$q = \frac{i_0}{\omega} \left[ -\cos \frac{2\pi}{T}(T) - \left( -\cos \frac{2\pi}{T}(0) \right) \right]$$

$$q = \frac{i_0}{\omega} \left[ -\cos 2\pi - \left( -\cos 0 \right) \right]$$

$$q = \frac{i_0}{\omega} (-1 - (-1))$$

$$q = \frac{i_0}{\omega} (-1 + 1)$$

$$q = 0$$

$$i_{av} = \frac{\Delta q}{\Delta t}$$

$$i_{av} = 0$$

IMP

for half cycle ( $0 - T/2$ )

$$i = \frac{dq}{dt}$$

$$dq = i \cdot dt$$

Int. both sides . . .

$$\int dq = \int_{0}^{T/2} i \cdot dt$$

$$q = \int_{0}^{T/2} i_0 \sin \omega t \cdot dt$$

$$q = i_0 \int_{0}^{T/2} \sin \omega t \cdot dt$$

$$q = i_0 \left[ -\frac{\cos \omega t}{\omega} \right]_0^{T/2}$$

$$q = \frac{i_0}{\omega} \left[ -\cos \frac{2\pi}{T} \times \frac{T}{2} - \left( -\cos \frac{2\pi}{T} \times 0 \right) \right]$$

$$q = \frac{i_0}{\omega} \left[ -\cos \pi - (-\cos 0) \right]$$

$$q = \frac{i_0}{\omega} \left[ -(-1) - (-1) \right]$$

$$q = \frac{i_0}{\omega} [ +1 + 1 ]$$

$$q = \frac{2i_0}{2\pi} = \frac{i_0 T}{\pi}$$

$$i_{av} = \frac{\Delta q}{\Delta t} = \frac{i_0 T}{\pi T/2} = \frac{2}{\pi} i_0$$

214

$$i_{av} = \frac{2}{\pi} i_0 = 0.637 i_0$$




## RMS Value of AC (RVSN)

It is the constant current which produces the same heating effect in a given resistor as it produces by the given AC when passed for same time

- Root Mean Square
- Virtual Value
- Effective Value
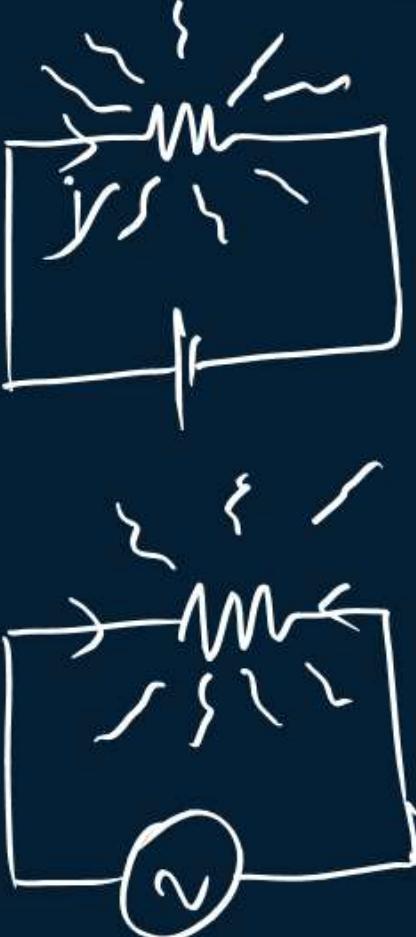
$$i_{\text{rms}}$$
$$i_v$$
$$i_{\text{eff}}$$



~~T.M.Q~~

$$H = i^2 R t$$

$$dH = i^2 R dt$$

Int. both sides . . .

$$\int dH = \int i^2 R dt$$

$$H = \int_0^T (i_0 \sin \omega t)^2 R dt$$

$$i_{rms}^2 R T = \int_0^T i_0^2 \sin^2 \omega t R dt$$

$$i_{rms}^2 R T = i_0^2 R \int_0^T \sin^2 \omega t dt$$

$$i_{rms}^2 = \frac{i_0^2}{T} \int_0^T \sin^2 \omega t dt$$

$$H = i_{rms}^2 R T$$

$$i_{rms} = \sqrt{\frac{i_0^2}{T} \int_0^T \sin^2 \omega t dt}$$

$$\int_0^T \sin^2 \omega t dt$$

$$\int_0^T \frac{1 - \cos 2\omega t}{2} dt$$

$$\frac{1}{2} \left( \int_0^T 1 dt - \int_0^T \cos 2\omega t dt \right)$$

$$\sin^2 \theta = \frac{1 - \cos 2\theta}{2}$$

eq ①

$$\frac{1}{2} \left[ [t]_0^T - \left[ \frac{\sin 2\omega t}{2\omega} \right]_0^T \right]$$

$$\frac{1}{2} \left[ (T - 0) - \left[ \sin \frac{2 \times 2\pi}{2\omega} \right] \right]$$

$$\frac{1}{2} \left[ T - \frac{1}{2\omega} \left[ \sin 4\pi - \sin 0 \right] \right]$$

$$\frac{1}{2} [T - 0] = \frac{T}{2}$$

Put this Value in Eq ① ..

$$i_{rms} = \sqrt{\frac{i_0^2}{T} \cdot \frac{\pi}{2}}$$

Ans\*

$$i_{rms} = \frac{i_0}{\sqrt{2}} = 0.707 i_0$$



## Form Factor



NEET/JEE/CUET

$$= \frac{i_{rms}}{i_{av}} \rightarrow \text{full cycle } (0-T)$$
$$i_{av} \rightarrow \text{half cycle } (0-T/2)$$

$$\frac{i_{rms}}{i_{av}} = \frac{\cancel{i_0}}{\sqrt{2}}$$
$$= 1.11$$

$$i_{av} = \frac{2}{\pi} \cancel{i_0}$$

$$\boxed{\frac{i_{rms}}{i_{av}} = 1.11}$$



# Homework

UDAY 2025

Notes → Uniform cm : SHM  
Videos - 1 lec +  $\frac{1}{2}$  lec

Derivations x 3 → 1 Fair


Oscillations - 1.5-2h → 2 Rough

6-7 hr





# PARISHRAM

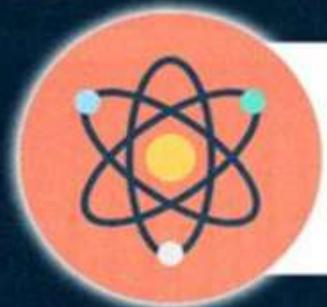

2026


Lecture - 02

Alternating Current

PHYSICS

Lecture - 2

BY - RAKSHAK SIR

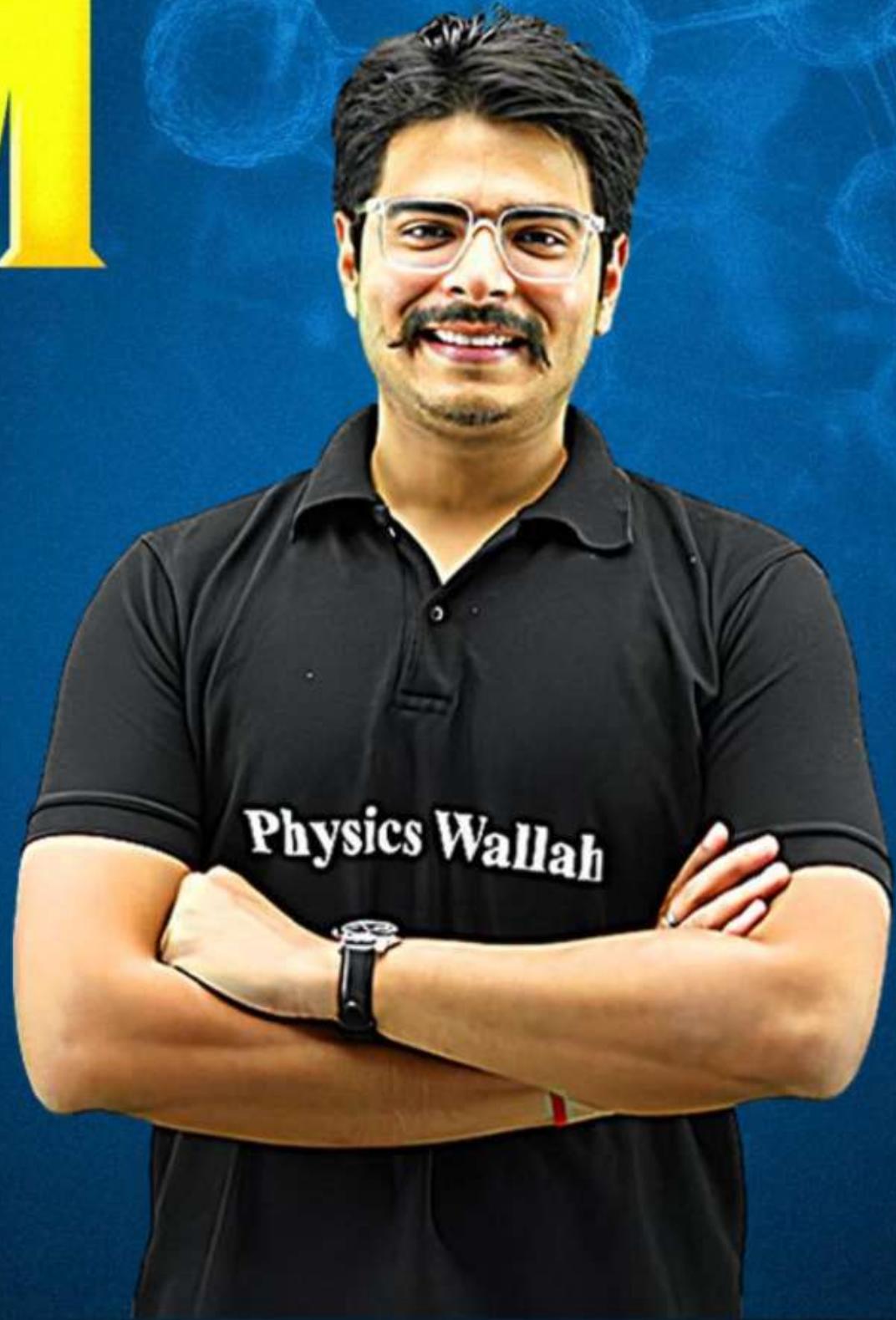

# Topics *to be covered*

- 1 AC Source Connected to  $R, L, C$ .
- 2 Phasors
- 3

## \* Some Mathematical RDx




$$\dot{i}_{av} = \frac{\int i \cdot dt}{\int dt} = \frac{\int i \cdot dt}{T}$$

$$i_{rms} = \sqrt{\frac{\int i^2 \cdot dt}{\int dt}} = \sqrt{\frac{\int i^2 \cdot dt}{T}}$$

$$\dot{i}_{av} = \langle i \rangle$$

$$V_{av} = \langle V \rangle$$

$$P_{av} = \langle P \rangle$$

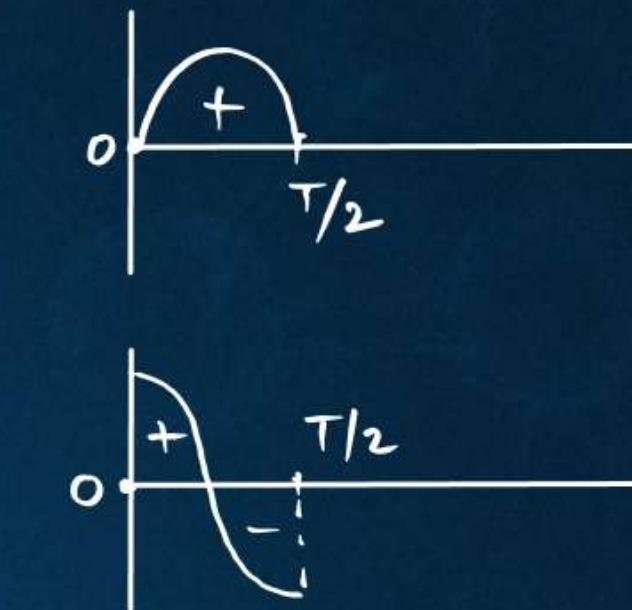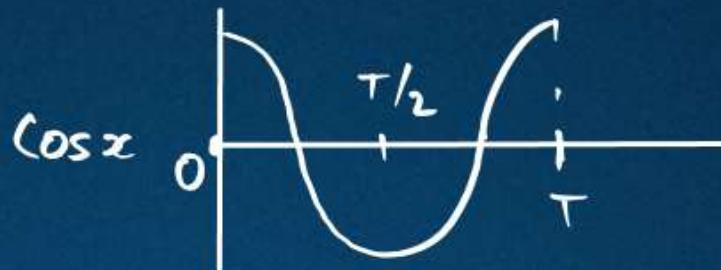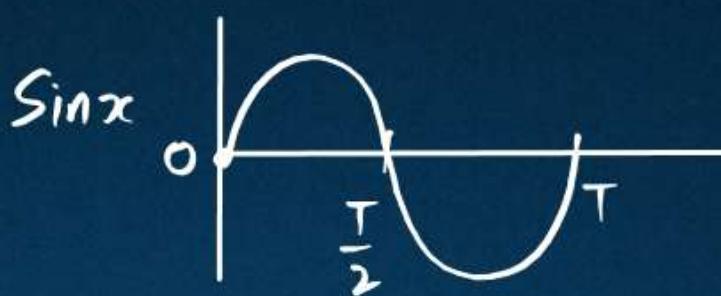

Full cycle :-

$$\langle \sin \omega t \rangle = 0$$

$$\langle \cos \omega t \rangle = 0$$

$$\langle \sin 2\omega t \rangle = 0$$

$$\langle \cos 2\omega t \rangle = 0$$

$$\langle \sin^2 \omega t \rangle = \frac{1}{2}$$

$$\langle \cos^2 \omega t \rangle = \frac{1}{2}$$

Half Cycle :-

$$\langle \sin \omega t \rangle = \frac{2}{\pi}$$

$$\langle \cos \omega t \rangle = 0$$

## QUESTION

$$\omega = 2\pi\nu$$

The time required for the 50 Hz sinusoidal source alternating current to reach its rms value from zero is

$$i = i_0 \sin \omega t$$

$$\omega t = \frac{\pi}{4}$$


$$i_{rms} = i_0 \sin \omega t$$

$$2\pi\nu t = \frac{\pi}{4}$$

$$i_{rms} = \frac{i_0}{\sqrt{2}}$$

$$\frac{1}{\sqrt{2}} = \sin \omega t$$

$$2\pi\nu t = \frac{\pi}{4}$$

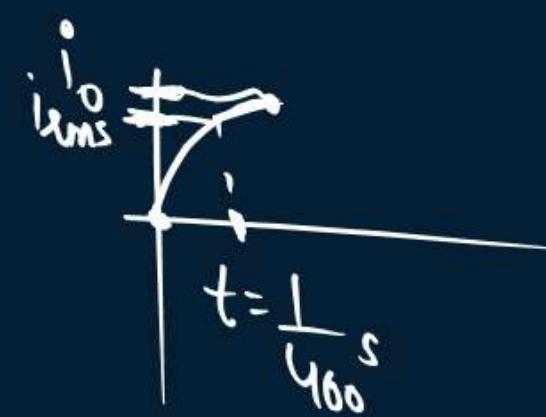

$$\sin \frac{\pi}{4} = \sin \omega t$$

$$t = \frac{1}{400} s$$



## Which is more dangerous? – 220 V DC or 220 V AC



↓  
Peak  
Value  
 $E_{DC}$   
Voltage = 220 V

↓  
RMS  
Value  
of  
A.C.  
Voltage = 220 V

$$E_{rms} = \sqrt{E_{DC}} = 220V$$

$$E_{rms} = \frac{E_0}{\sqrt{2}}$$

$$E_0 = \sqrt{2} \times E_{rms} = \sqrt{2} \times 220 = 311V$$



## Measurement of AC

M.C.

→ Galvanometer is best device to measure D.C.  
but Not A.C.

→ Hot-wire Galvanometer



## QUESTION

An alternating current is given by  $I = I_1 \cos \omega t + I_2 \sin \omega t$ . The ~~RMS~~ value of current is given by

**A**  $\frac{I_1 + I_2}{\sqrt{2}}$

**B**  $\frac{(I_1 + I_2)^2}{2}$

**C**  $\sqrt{\frac{I_1^2 + I_2^2}{2}}$

**D**  $\frac{\sqrt{I_1^2 + I_2^2}}{2}$

$$I = I_1 \cos \omega t + I_2 \sin \omega t$$

$$I^2 = (I_1 \cos \omega t + I_2 \sin \omega t)^2$$

$$I^2 = I_1^2 \cos^2 \omega t + I_2^2 \sin^2 \omega t + 2I_1 I_2 \sin \omega t \cos \omega t$$

$$I^2 = I_1^2 \frac{1}{2} + I_2^2 \frac{1}{2} + 0$$

$$I^2 = \frac{I_1^2}{2} + \frac{I_2^2}{2}$$

$$I^2 = \frac{I_1^2 + I_2^2}{2} \rightarrow I = \sqrt{\frac{I_1^2 + I_2^2}{2}}$$



## AC Source connected to Resistor

$$\boxed{V = V_0 \sin \omega t}$$

$$i = i_0 \sin \omega t$$

both  $V$  and  $i$   
are in same phase

$$\begin{aligned}\Delta\phi &= \phi_2 - \phi_1 \\ &= \omega t - \omega t\end{aligned}$$

$\Delta\phi = 0$   
(No Phase Diff)


$$iR = V_0 \sin \omega t$$

$$i = \left(\frac{V_0}{R}\right) \sin \omega t \quad \dots \textcircled{3}$$

Comparing eq ③ with  
General eq of A.C.

$$i = i_0 \sin \omega t$$

$$\boxed{i_0 = \frac{V_0}{R}}$$

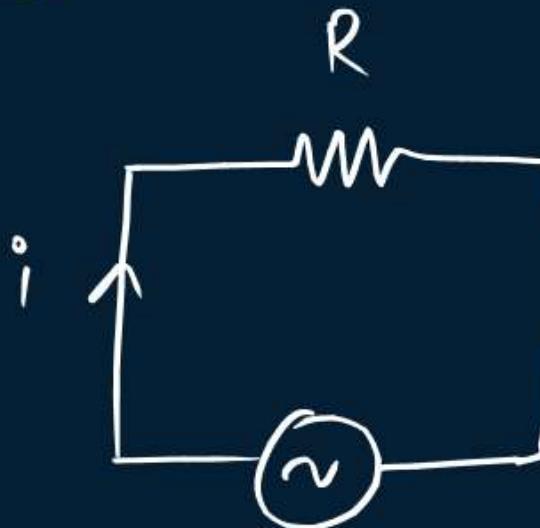


$$V = V_0 \sin \omega t \quad \dots \textcircled{1}$$

$$V = iR \quad \dots \textcircled{2}$$

Equate ① and ②

$$iR = V_0 \sin \omega t$$

\* Graph & Phasor

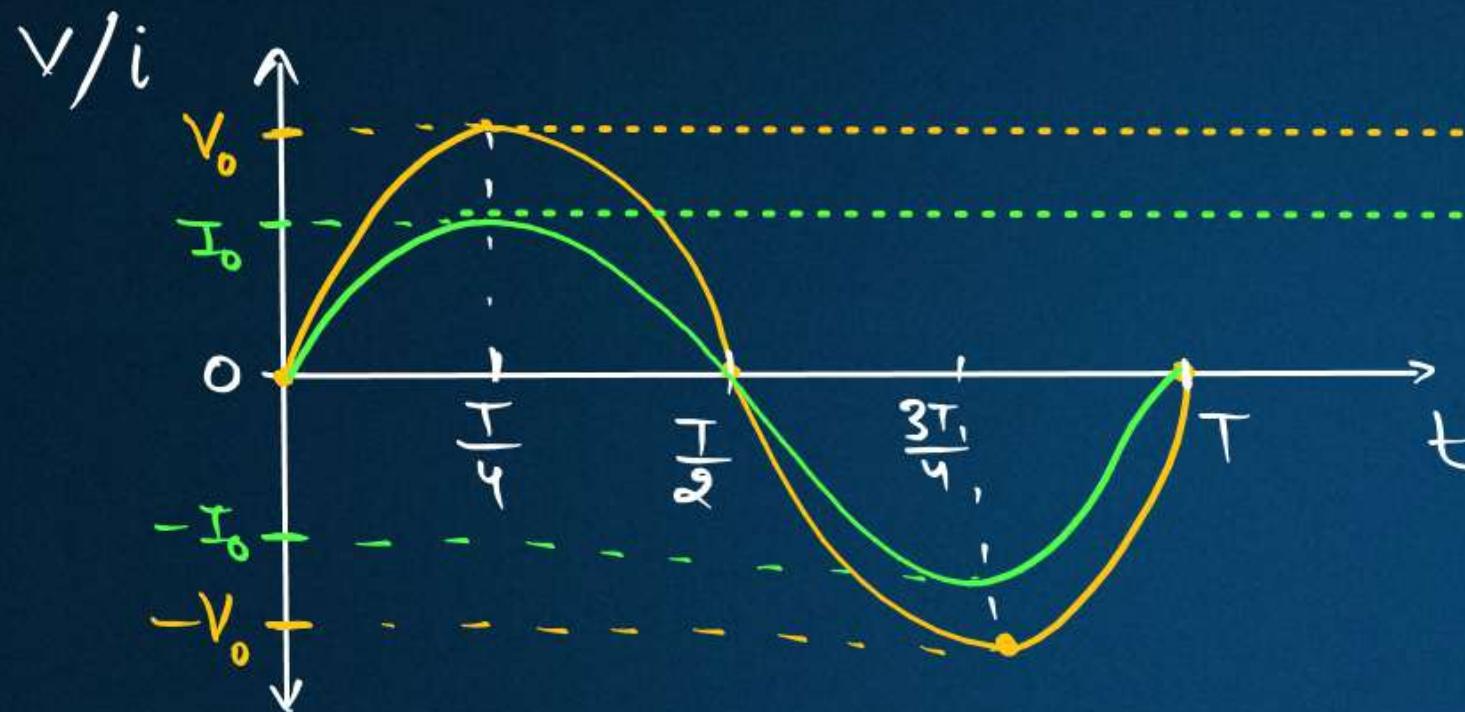


$$V = V_0 \sin \omega t$$

$$i = i_0 \sin \omega t$$

$$\left\{ \begin{array}{l} \omega t = \theta \\ \omega = \frac{\theta}{t} \end{array} \right\}$$

Phasor Diagram

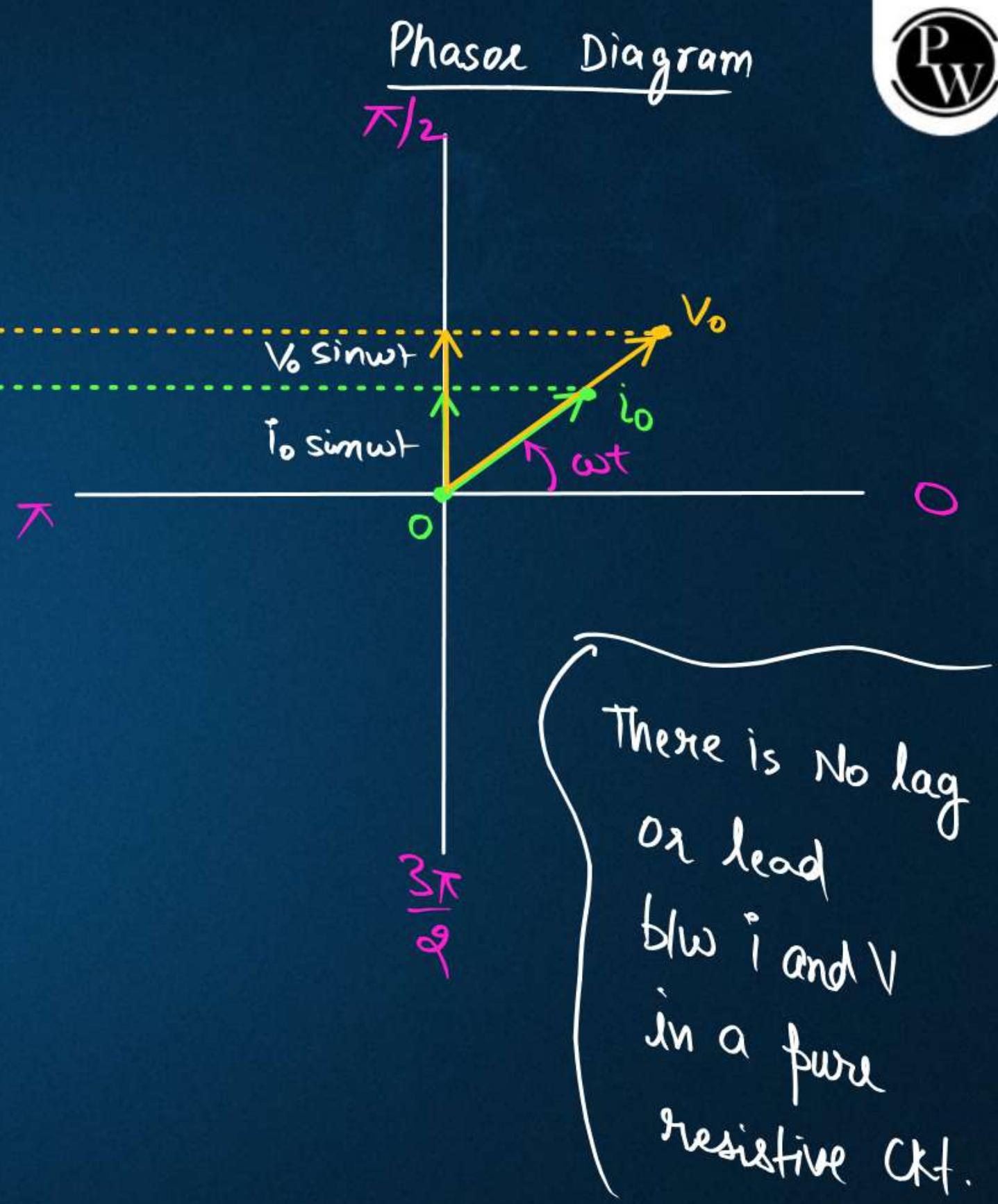

## \* Power Consumed



$$V = V_0 \sin \omega t$$

$$i = i_0 \sin \omega t$$

$$P = VI$$

$$\begin{aligned} P &= VI \\ &= V_0 \sin \omega t \cdot i_0 \sin \omega t \end{aligned}$$

$$P = V_0 i_0 \sin^2 \omega t$$

$$\begin{aligned} P_{av} &= \frac{\int P \cdot dt}{\int dt} \\ &= \frac{\int V_0 i_0 \sin^2 \omega t \cdot dt}{\int dt} \end{aligned}$$

$$P_{av} = V_0 i_0 \times \frac{1}{2}$$

$$P_{av} = \frac{V_0}{\sqrt{2}} \frac{i_0}{\sqrt{2}}$$

$$P_{av} = V_{rms} i_{rms}$$

Pure Resistive

$$\int \sin^2 \omega t \cdot dt = \frac{1}{2}$$



$$\sin(\theta_0 + \theta) = \cos \theta$$



# AC Source connected to Capacitor

→ Pure capacitive Ckt.

$$i = CV_0 \omega \cos \omega t$$

$$i = \underline{CV_0 \omega} \sin\left(\omega t + \frac{\pi}{2}\right)$$

$$i = i_0 \sin\left(\omega t + \frac{\pi}{2}\right)$$

$$V = V_0 \sin \omega t$$

$$\frac{q}{C} = V_0 \sin \omega t$$

$$q = CV_0 \sin \omega t$$

diff. both sides . . .

i has  $\frac{\pi}{2}$  phase diff ( $\Delta\phi$ )

than V


here, i leads V by  $\frac{\pi}{2}$

V lags i by  $\frac{\pi}{2}$

$$\frac{dq}{dt} = \frac{d(CV_0 \sin \omega t)}{dt}$$

$$i = CV_0 \cdot \cos \omega t \cdot \omega$$


$$i = CV_0 \omega \cos \omega t$$

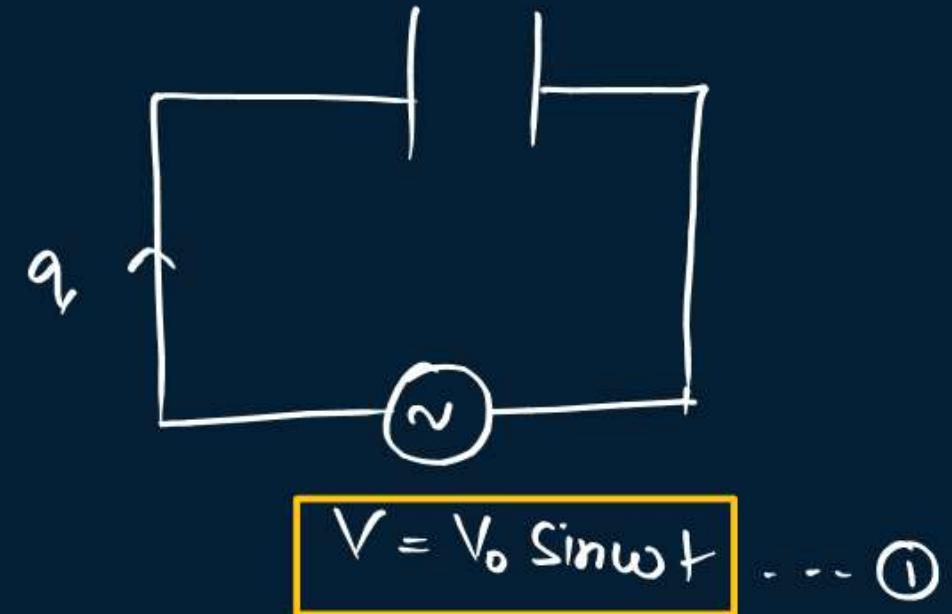

$$q = CV$$

$$V = \frac{q}{C} \quad \dots \textcircled{II}$$


\* Graph & Phasor

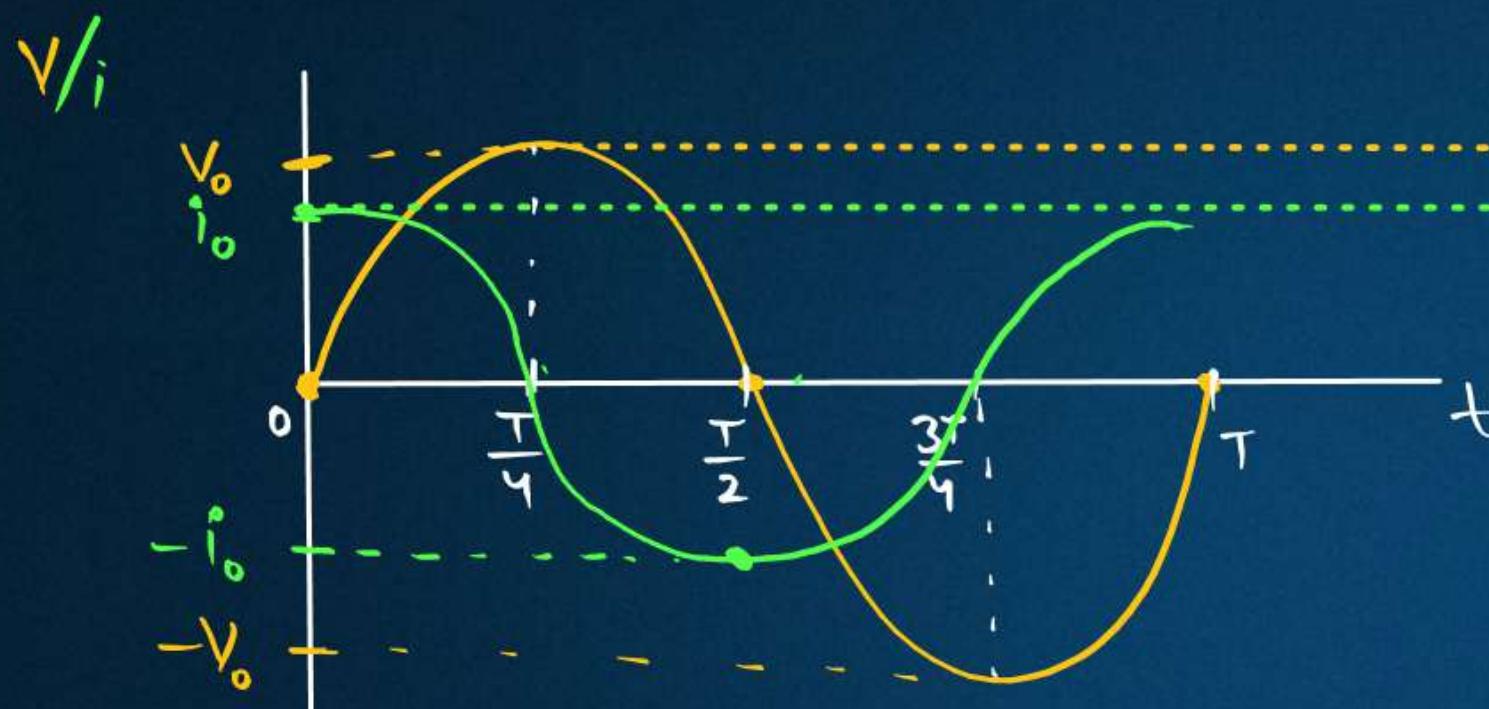

$$V = V_0 \sin \omega t$$

$$i = i_0 \sin \left( \omega t + \frac{\pi}{2} \right)$$
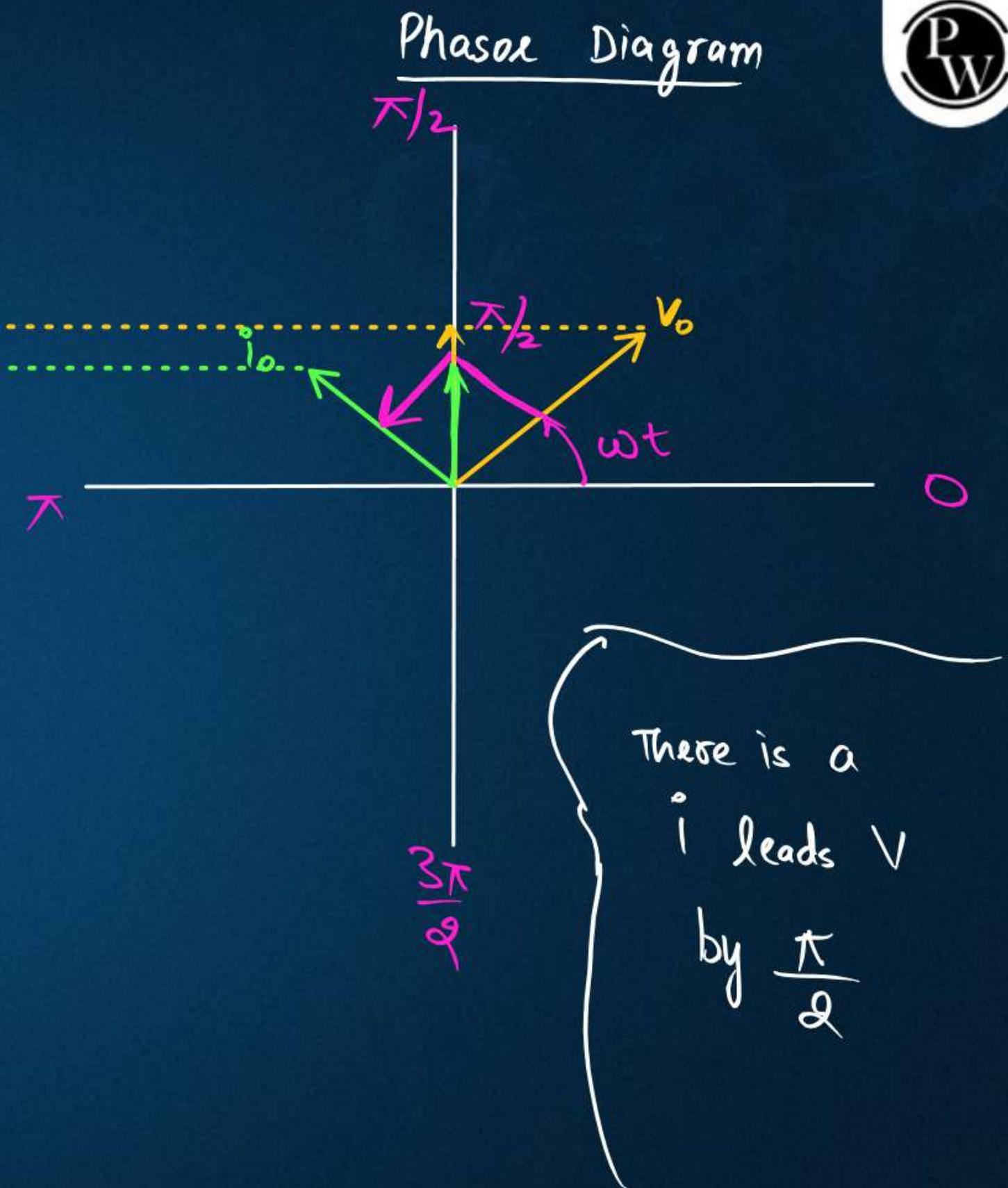
$$\left\{ \begin{array}{l} \omega t = \theta \\ \omega = \frac{\theta}{t} \end{array} \right\}$$



## Power

$$P = VI$$

$$\begin{aligned} P &= V_0 \sin(\omega t) \times i_0 \sin\left(\omega t + \frac{\pi}{2}\right) \\ &= V_0 i_0 \sin \omega t \cdot \cos \omega t \end{aligned}$$

$$P_{av} = V_0 i_0 \langle \sin \omega t \rangle \langle \cos \omega t \rangle$$

$$P_{av} = V_0 i_0 \times 0$$

$P_{av} = 0$

$$\cos \theta = \sin(90 - \theta), \quad -\sin \theta = \sin(-\theta)$$



## AC Source connected to Inductor

$$i = \frac{V_0}{\omega L} (-\cos \omega t)$$

$$L \frac{di}{dt} = V_0 \sin \omega t$$

$$i = \frac{V_0}{\omega L} \left( -\sin \left( \frac{\pi}{2} - \omega t \right) \right)$$

$$di = \frac{V_0}{L} \sin \omega t \cdot dt$$

$$i = \left( \frac{V_0}{\omega L} \right) \sin \left( -\frac{\pi}{2} + \omega t \right)$$

$$i = i_0 \sin \left( \omega t - \frac{\pi}{2} \right)$$

$i$  lags behind  $V$  by  $\pi/2$


$V$  leads  $i$  by  $\frac{\pi}{2}$

Int. both sides . . .

$$\int di = \int \frac{V_0}{L} \sin \omega t \cdot dt$$

$$i = \frac{V_0}{L} \int \sin \omega t \cdot dt$$
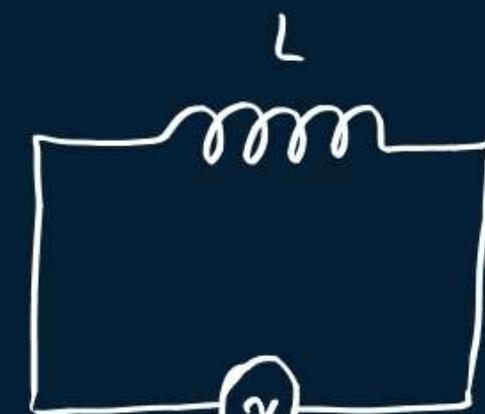
$$i = \frac{V_0}{L} \left( -\frac{\cos \omega t}{\omega} \right)$$




$$V = V_0 \sin \omega t \quad \dots \textcircled{1}$$

$$\epsilon = -L \frac{di}{dt} \quad \dots \textcircled{2}$$

$$V = \epsilon$$

$$V_0 \sin \omega t = -L \frac{di}{dt}$$


\* Graph & Phasor

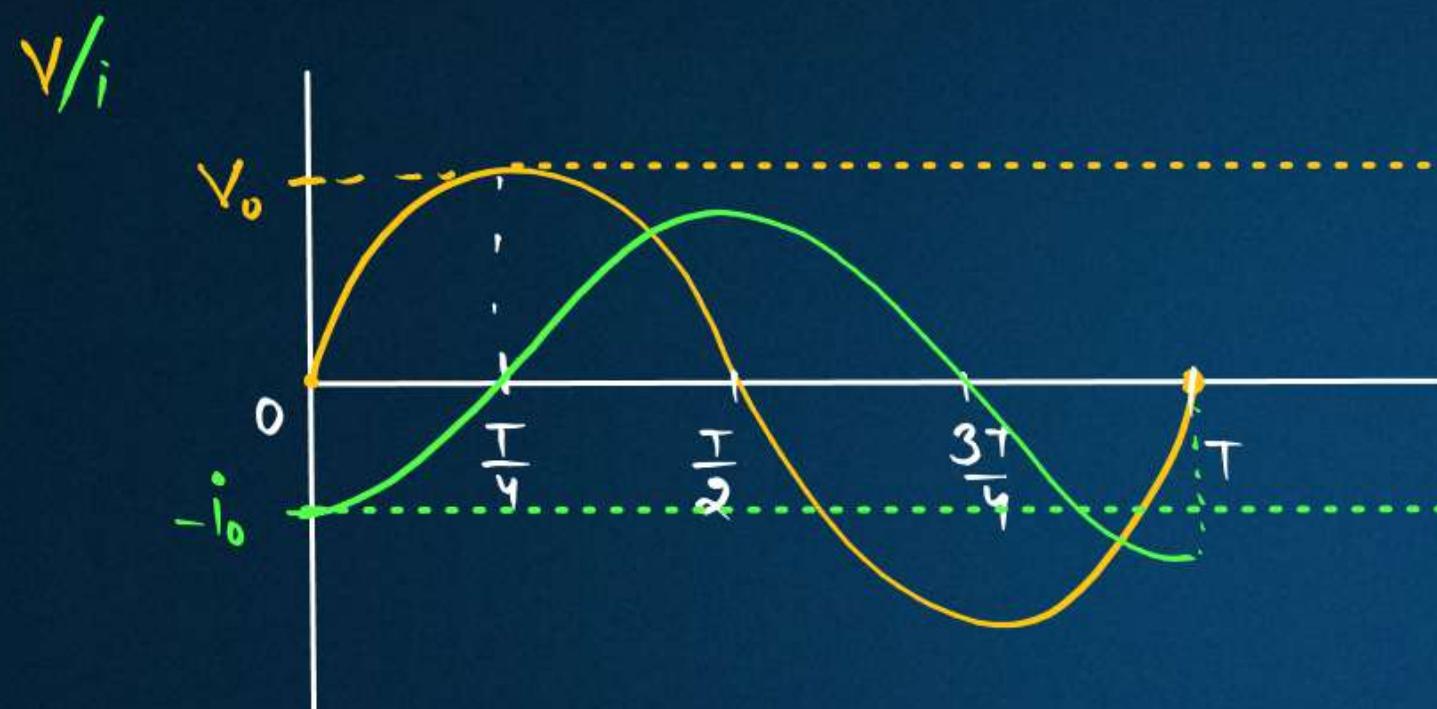

$$V = V_0 \sin \omega t$$

$$i = i_0 \sin\left(\omega t - \frac{\pi}{2}\right) \quad \left\{ \begin{array}{l} \omega t = \theta \\ \omega = \frac{\theta}{t} \end{array} \right.$$

Phasor Diagram

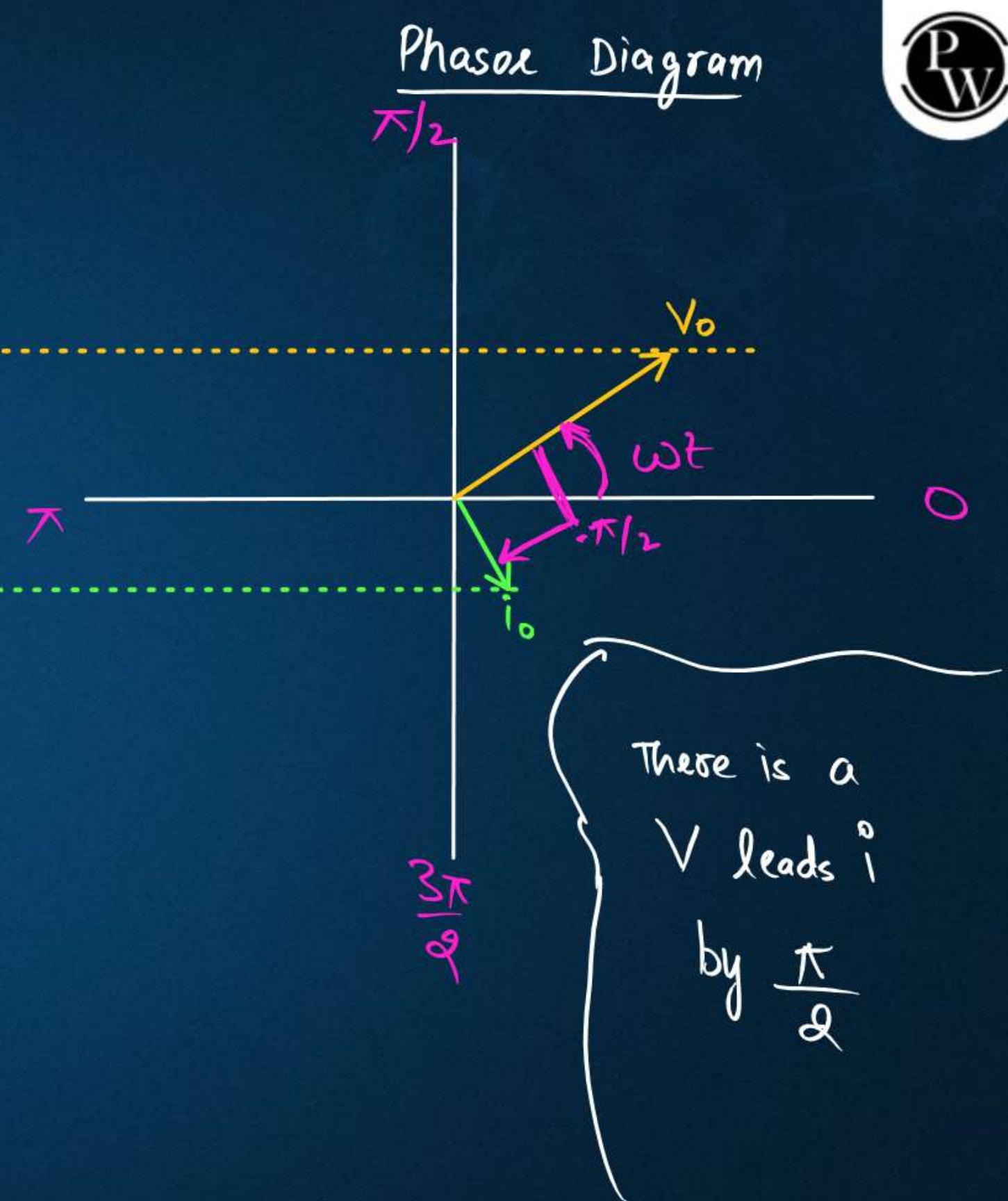


Power in pure inductive circuit.

$$\begin{aligned} P &= V I \\ &= V_0 \sin \omega t \quad i_0 \sin \left( \omega t - \frac{\pi}{2} \right) \\ &= V_0 \sin \omega t (-i_0 \cos \omega t) \end{aligned}$$

$$P_{av} = -V_0 i_0 \langle \sin \omega t \times \cos \omega t \rangle$$

$$\boxed{P_{av} = 0}$$

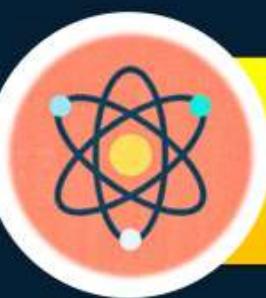

## Watt-less Currents

↓  
Currents in  
purely inductive  
as well as capacitive

Circuits,  
do not dissipate

Power Averagely

$$P_{av} = 0$$

$i \rightarrow$  Watt-less current



# Homework

Notes

Likh Ke Practice x 1

DPP Try



# PARISHRAM



2026


Lecture - 03

## Alternating Current

PHYSICS

Lecture - 3

BY - RAKSHAK SIR



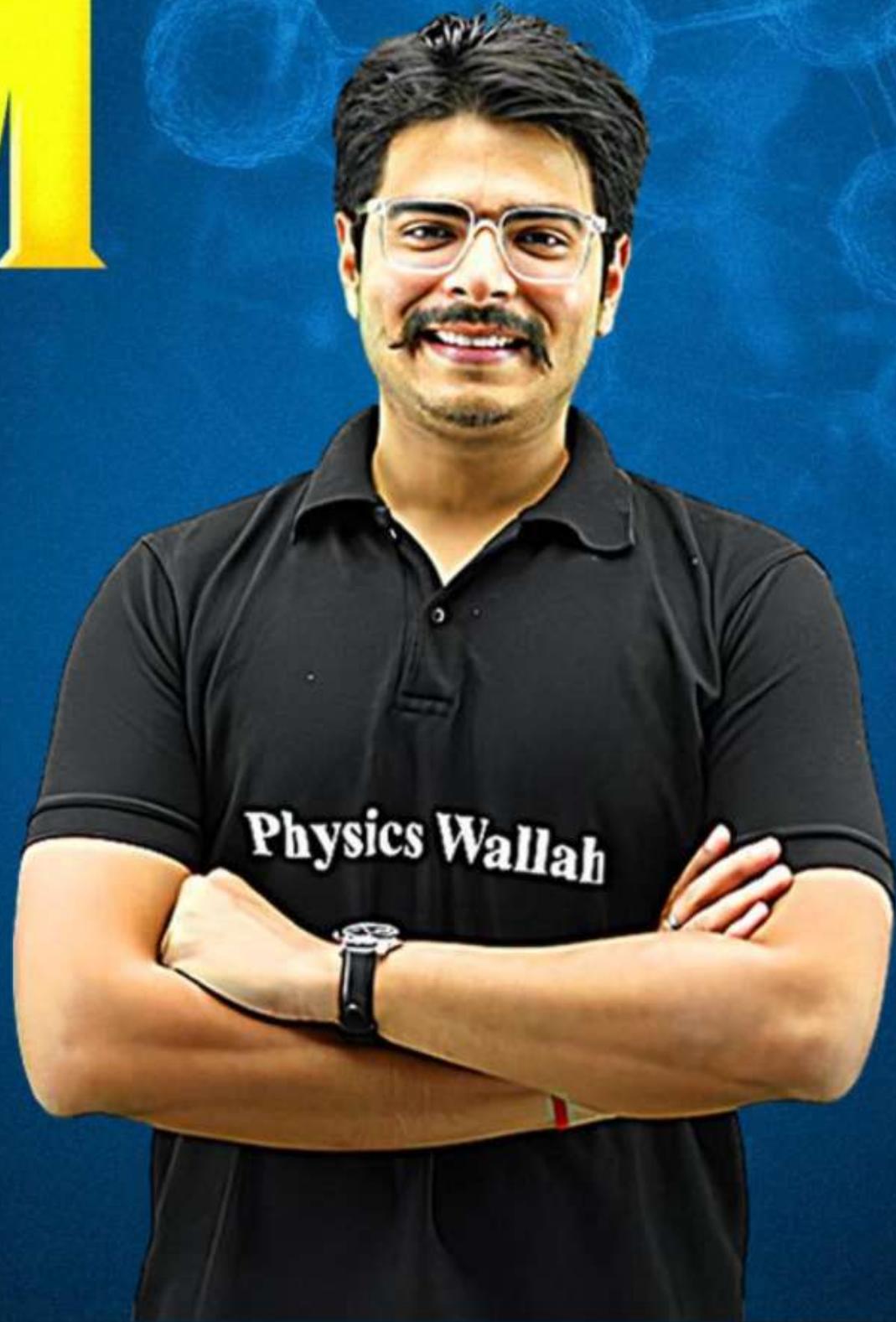


# Topics *to be covered*

- 1 Series L,C,R Circuit
- 2 Resonance
- 3



# AC Source connected to Resistor

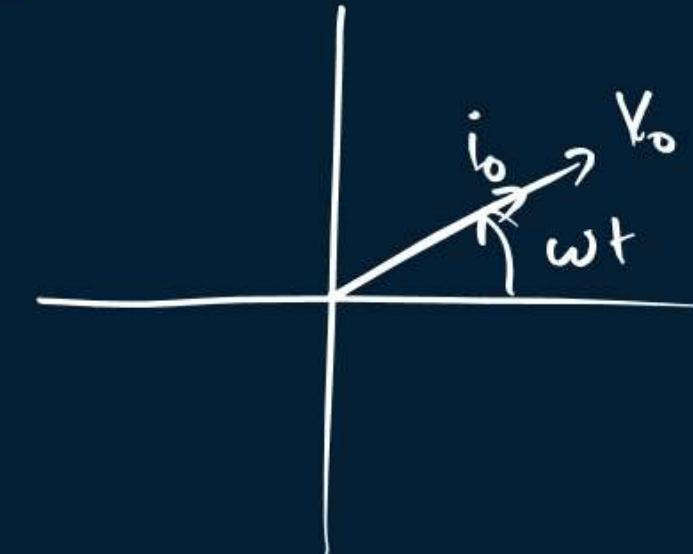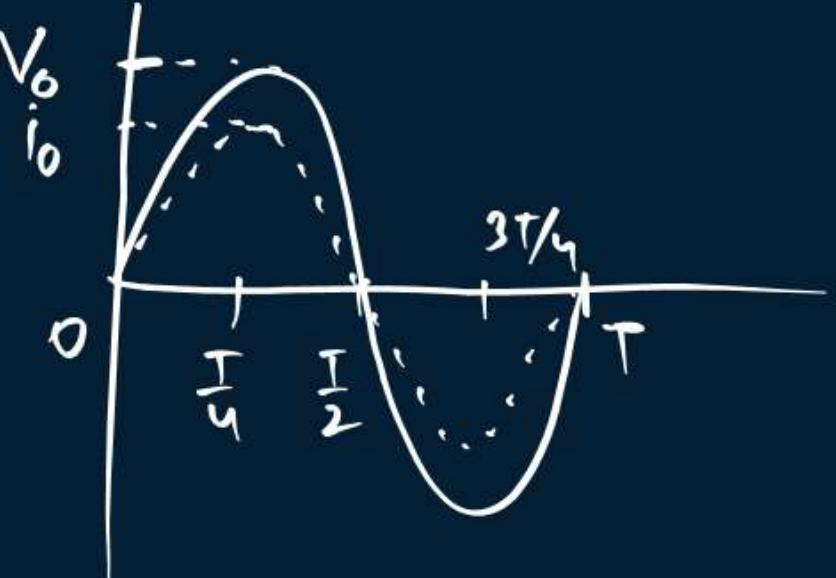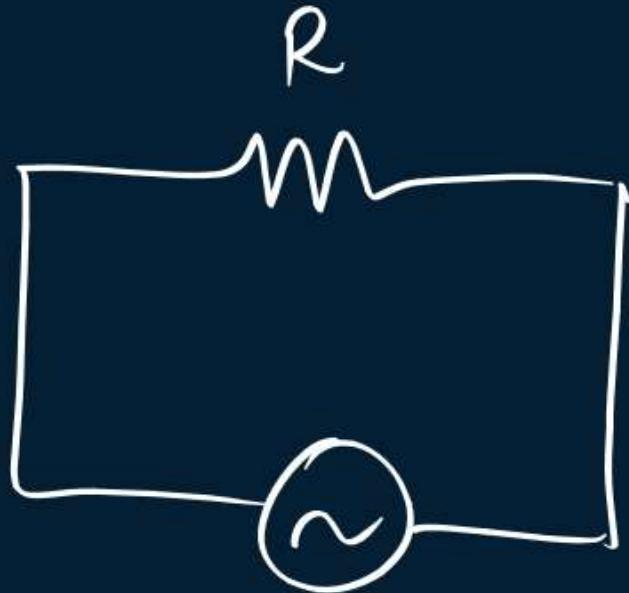

$$V = V_0 \sin \omega t$$

$$\overset{\circ}{I} = \left( \frac{V_0}{R} \right) \sin \omega t$$

$$\overset{\circ}{I} = I_0 \sin \omega t$$




Same Phase

$$I_0 = \frac{V_0}{R}$$

$$P_{av} = V_{rms} \cdot I_{rms}$$



# AC Source connected to Capacitor

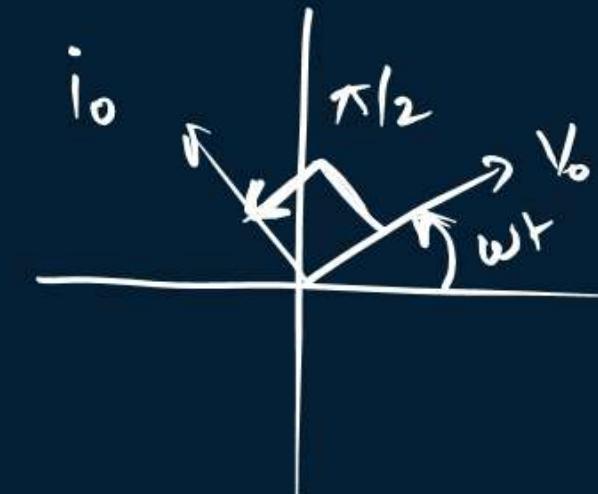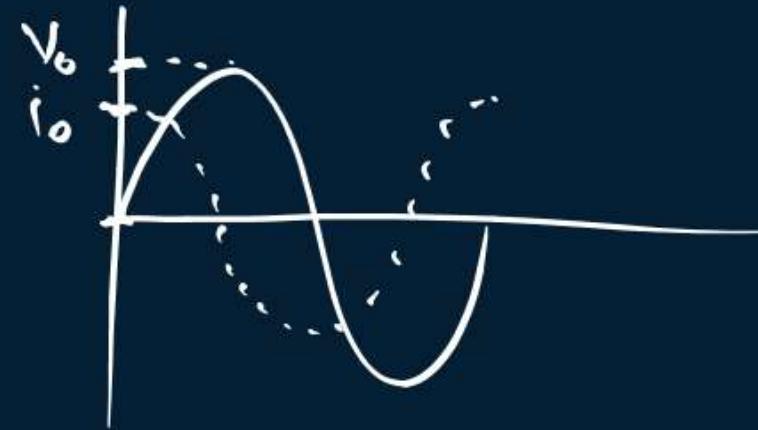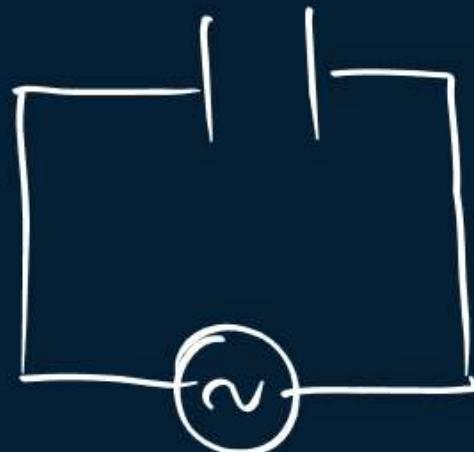

$$V = V_0 \sin \omega t$$

$$i = \omega C V_0 \sin\left(\omega t + \frac{\pi}{2}\right)$$

$$i = i_0 \sin\left(\omega t + \frac{\pi}{2}\right)$$




i leads  
v by  $\frac{\pi}{2}$

$$i_0 = \omega C V_0$$

$$P_{av} = 0$$



# AC Source connected to Inductor

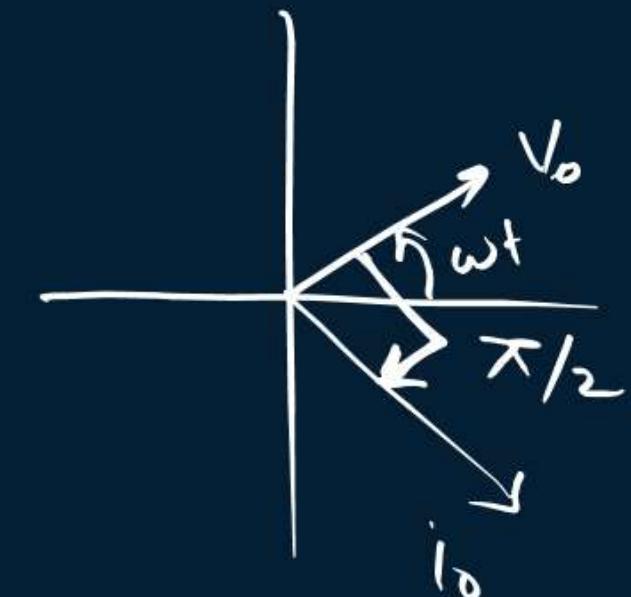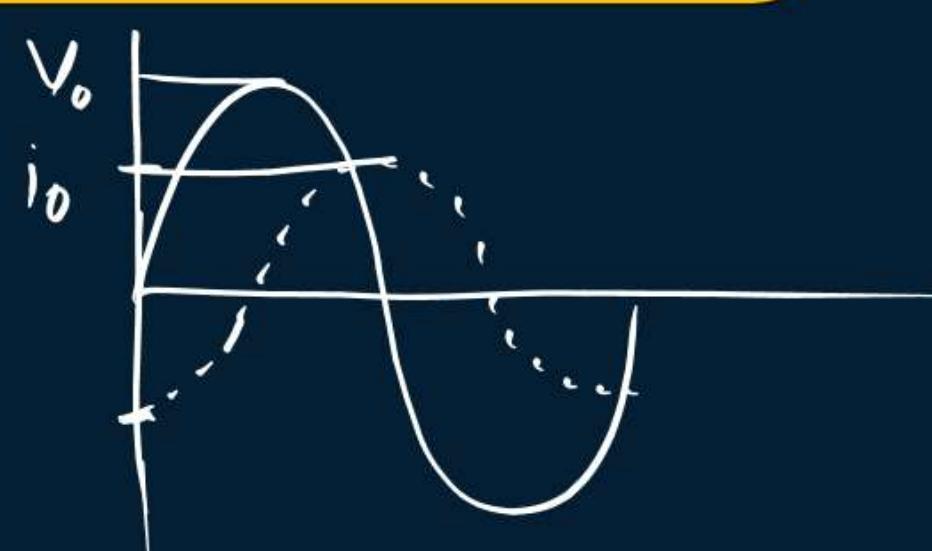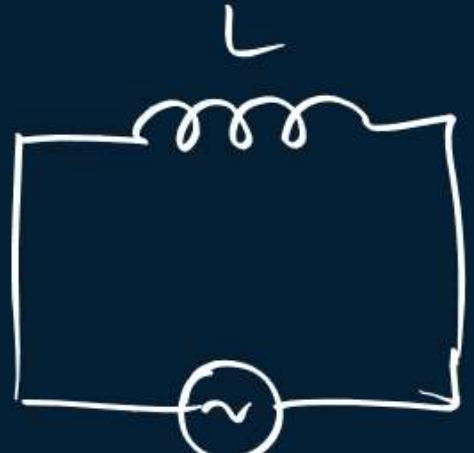

V leads i by  $\left(\frac{\pi}{2}\right)$

$$V = V_0 \sin \omega t$$

$$\dot{i} = \left[ \frac{V_0}{\omega L} \right] \sin \left( \omega t - \frac{\pi}{2} \right)$$

$$\ddot{i} = i_0 \sin \left( \omega t - \frac{\pi}{2} \right)$$

$$i_0 = \frac{V_0}{\omega L}$$

$$P_{av} = 0$$

# Variation of Reactance with frequency



Inductive  
reactance

Capacitive  
reactance

$$\dot{i}_0 = \frac{\dot{V}_0}{\omega L}$$

→ The opposition  
offered by

an inductor  
(connected to  
an AC ckt.)

$$\dot{V}_0 = \dot{i}_0(\omega L)$$

$$\dot{V}_0 = \dot{i}_0(X_L)$$

$\dot{V} = IR$

$$\rightarrow X_L = \omega L$$

→ Ohm ( $\Omega$ )

→ The opposition  
offered by a  
capacitor connected  
to an A.C. source

$$\rightarrow X_C = \frac{1}{\omega C}$$

→ Ohm ( $\Omega$ )

$$\dot{i}_0 = \omega C \dot{V}_0$$

$$\dot{V}_0 = \left( \frac{1}{\omega C} \right) \dot{i}_0$$

$$\dot{V}_0 = \dot{i}_0 X_C$$

$$\dot{V} = IR$$

$$* X_L = \omega L$$

$$X_L = 2\pi\nu L$$

$$\omega = \frac{2\pi}{T}$$

$$\omega = 2\pi\nu$$


$$* X_C = \frac{1}{\omega C}$$

$$X_C = \frac{1}{2\pi\nu C}$$

$$X_L \propto \nu$$

OR


$$X_L \propto \omega$$

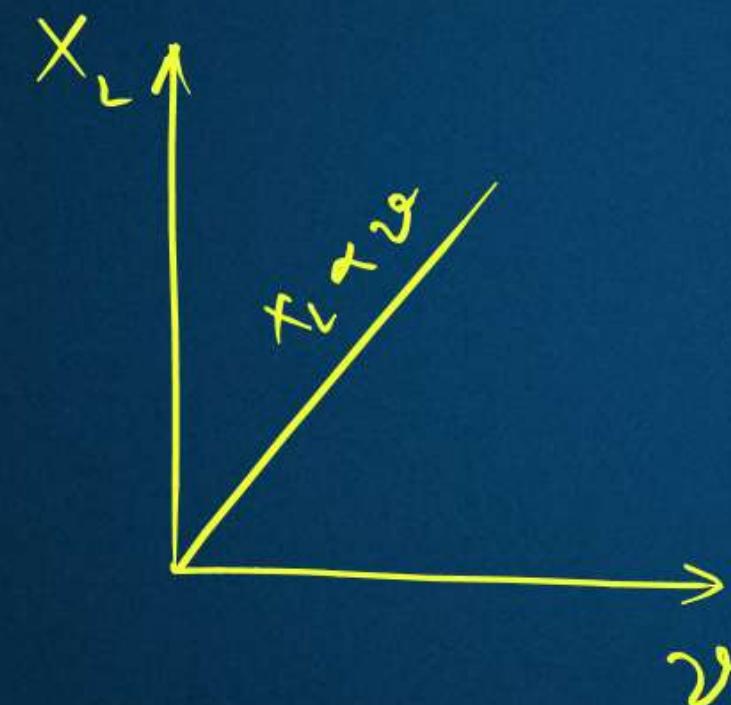


$$X_C \propto \frac{1}{\nu}$$

OR

$$X_C \propto \frac{1}{\omega}$$

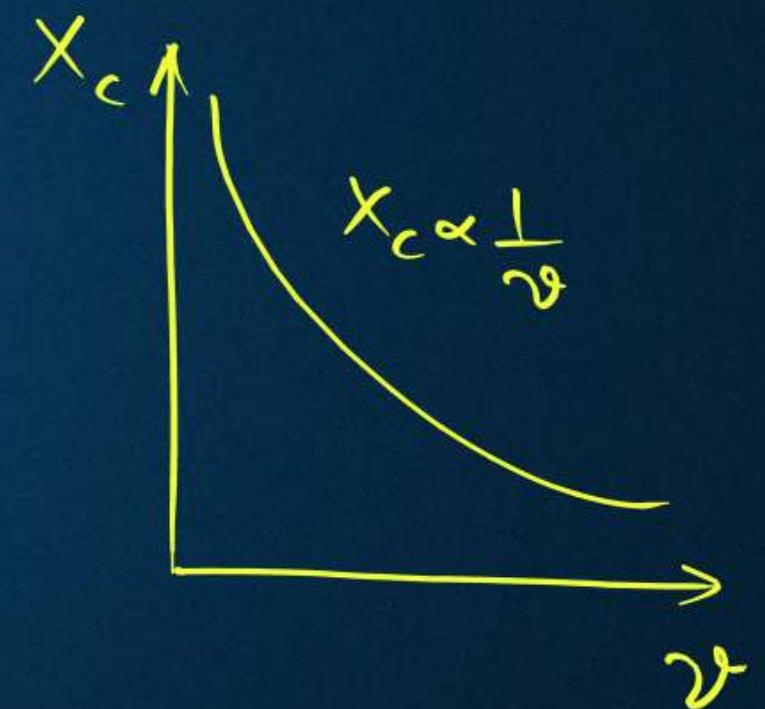

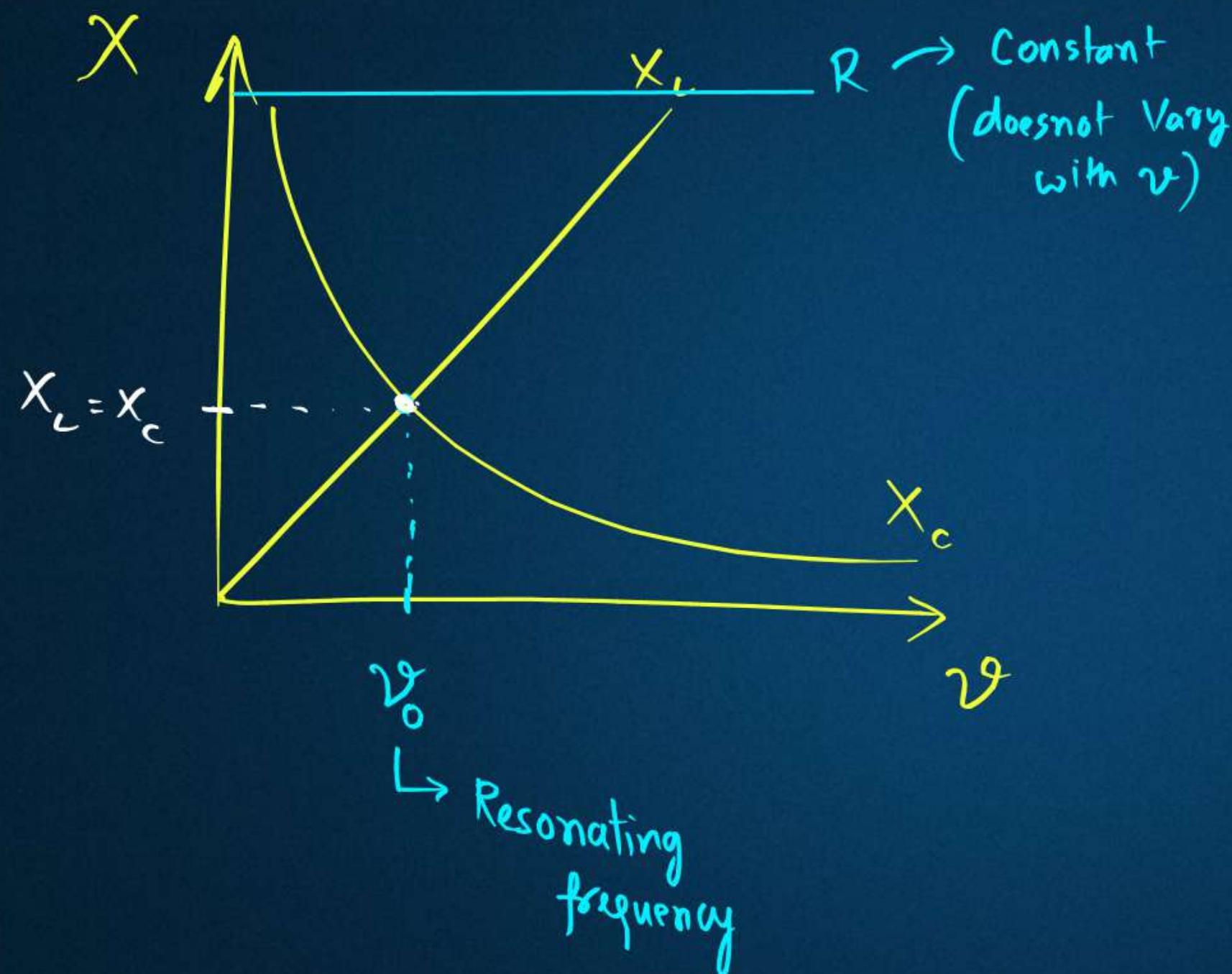Combined Graph

**QUESTION**

The reactance of a capacitor of capacitance C is X. If both the frequency and capacitance be doubled, then new reactance will be [CBSE AIPMT 2001]

A X

B 2X

C 4X

D ~~X/4~~

$$X_C = \frac{1}{\omega C}$$


$$X_C = \frac{1}{2\pi\nu C}$$

$$X'_C = \frac{1}{2\pi 2\nu 2C} = \frac{1}{4} \left( \frac{1}{2\pi\nu C} \right)$$

$$X'_C = \frac{1}{4} X_C$$

$$X'_C = \frac{X}{4}$$

# High pass and Low pass filter

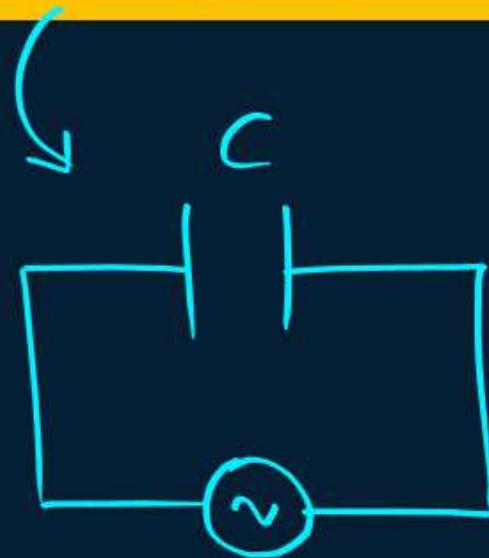


DC :  $\mathcal{V} = 0$   
 $\omega = 0$   
 $X_C = \frac{1}{\omega C} = \frac{1}{0} = \infty$   
 $i = 0$

AC :  $\mathcal{V} \rightarrow \text{Very high } \approx \infty$

$\omega \rightarrow \infty$

$$X_C = \frac{1}{\omega C} = \frac{1}{\infty} = 0$$
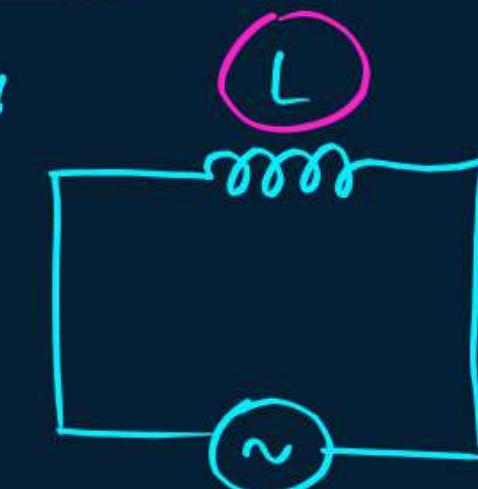
$$X_C = 0, i \rightarrow \infty (\text{Very high})$$



D.C. :  $\mathcal{V} = 0$   
 $\omega = 0$   
 $X_L = \omega L$   
 $X_L = 0$   
 $i \rightarrow \infty$

A.C. :  $\mathcal{V} \rightarrow \text{Very high } \approx \infty$

$\omega \rightarrow \infty$

$$X_L = \omega L = \infty$$


$$i = 0$$



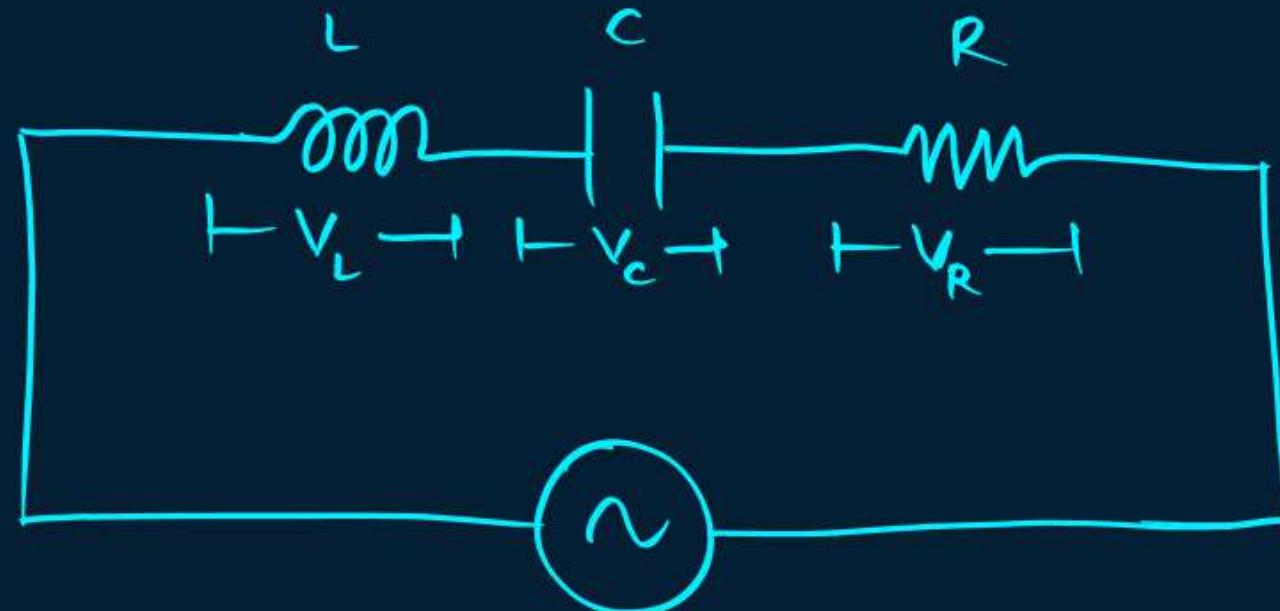
# Series LCR Circuit with AC



$$\vec{V}_{\text{net}} = \vec{V}_L + \vec{V}_C + \vec{V}_R \quad \times$$



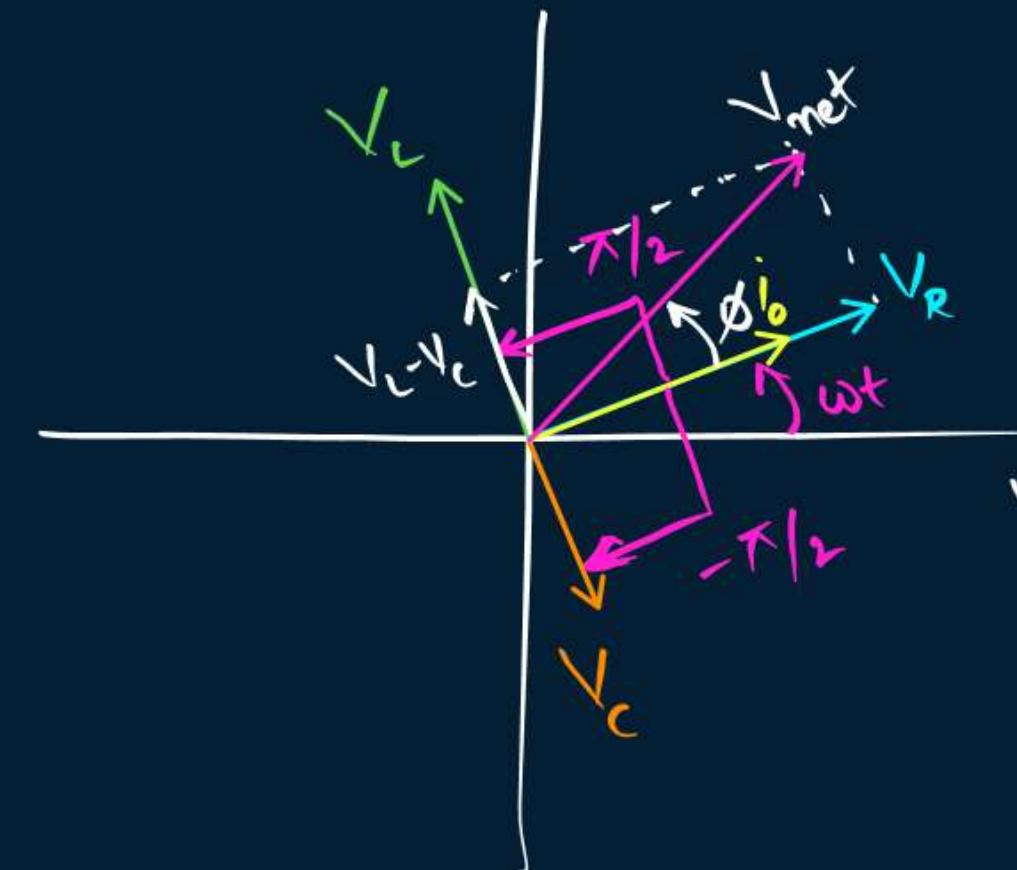$V = V_0 \sin \omega t$   
 $i = i_0 \sin \omega t$   
 Same phase with  $i \leftarrow V_R = V_0 \sin \omega t$   
 lag  $\leftarrow V_C = V_0 \sin \left( \omega t - \frac{\pi}{2} \right)$   
 lead  $\leftarrow V_L = V_0 \sin \left( \omega t + \frac{\pi}{2} \right)$





↳ We will use Phasors

Suppose  $V_L > V_C$

$$V_L - V_C$$

$$V_{\text{net}} = \sqrt{V_R^2 + (V_L - V_C)^2}$$
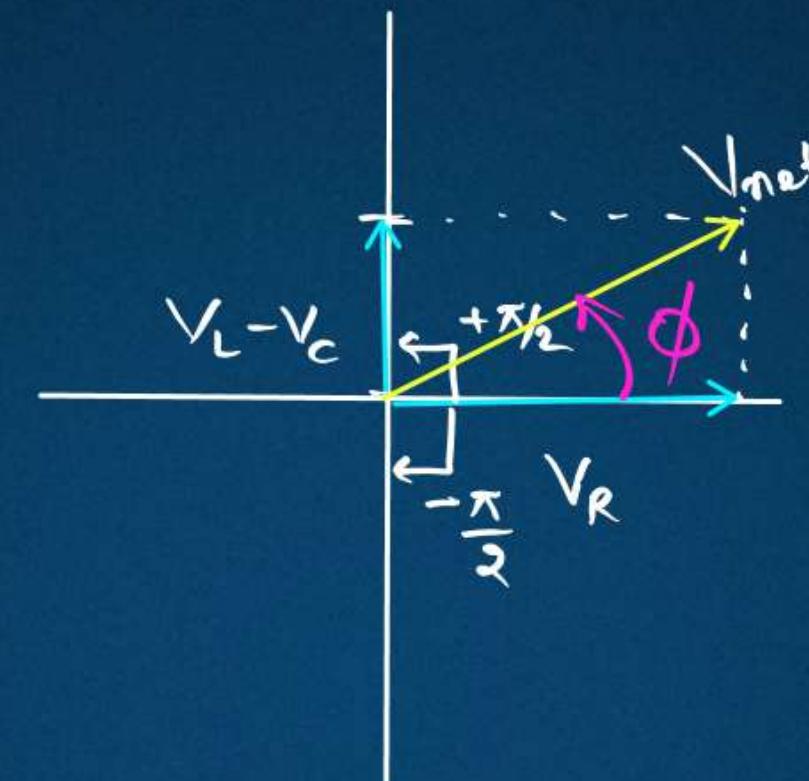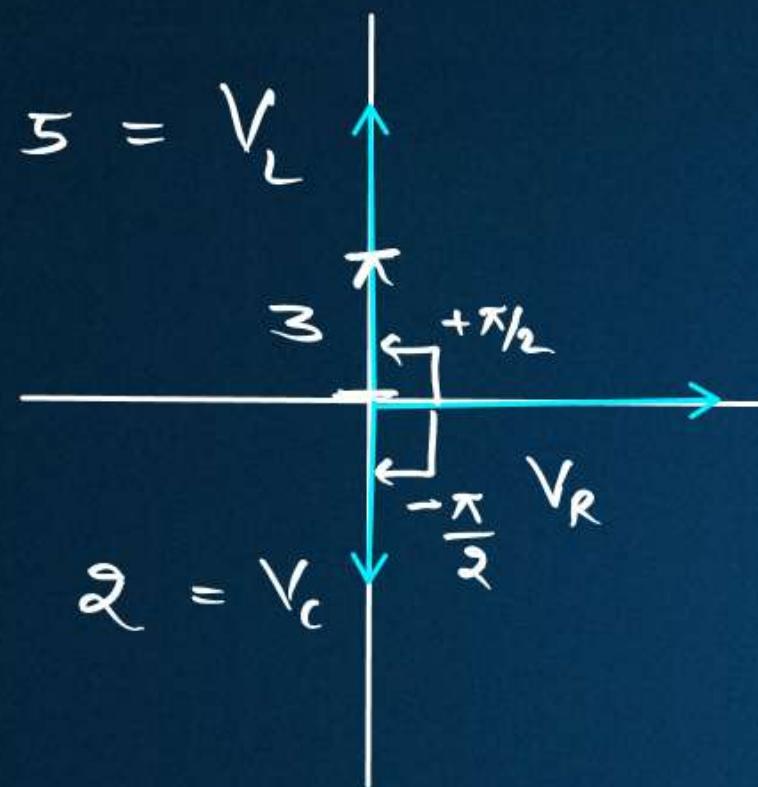
$$V_{\text{net}} = \sqrt{V_R^2 + (V_L - V_C)^2}$$



$$\tan \phi = \frac{P}{B} = \frac{V_L - V_C}{V_R}$$

$$\tan \phi = \frac{V_L - V_C}{V_R}$$

$$V_{\text{net}} = V_0 \sin(\omega t + \phi)$$

$$I = I_0 \sin \omega t$$

$$\cos \phi = \frac{V_R}{V_{\text{net}}}$$

$$V_{\text{net}} = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$V_{\text{net}}^2 = V_R^2 + (V_L - V_C)^2$$

$$(I \cdot Z)^2 = (I R)^2 + (I X_L - I X_C)^2$$

~~$$Z^2 = R^2 + (X_L - X_C)^2$$~~

$$Z^2 = R^2 + (X_L - X_C)^2$$

Impedance

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Impedance is the total opposition offered by Series L-C-R circuit connected to An A.C. Source

$$\rightarrow Z$$

SI unit  $\rightarrow$  ohm ( $\Omega$ )

$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$


$$\tan \phi = \frac{X_L - X_C}{R}$$

$$\cos \phi = \frac{R}{Z}$$

Power factor



## Power consumed in series LCR circuit

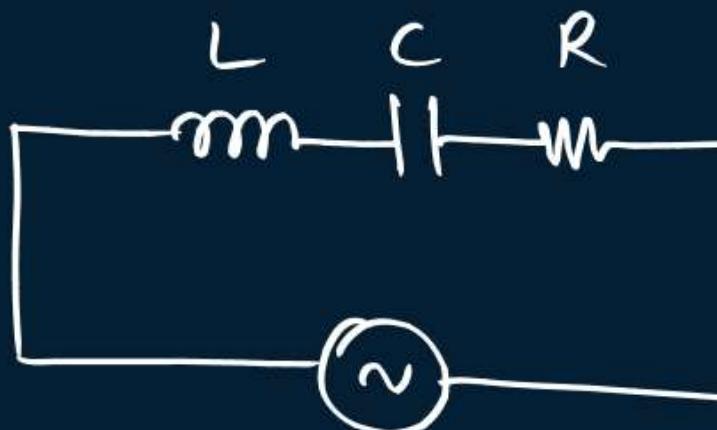

$$V = V_0 \sin(\omega t + \phi)$$

$$i = i_0 \sin \omega t$$

$$P = Vi$$

$$P = V_0 \sin(\omega t + \phi) i_0 \sin \omega t$$

$$P = V_0 i_0 \sin \omega t \underbrace{\sin(\omega t + \phi)}$$

$$P = V_0 i_0 \sin \omega t [\sin \omega t \cos \phi + \cos \omega t \sin \phi]$$

$$P = V_0 i_0 [\sin^2 \omega t \cos \phi + \sin \omega t \cos \omega t \sin \phi]$$

$$P = V_0 i_0 [\sin^2 \omega t \cos \phi + (\frac{1}{2} \sin \omega t \cos \omega t) \sin \phi]$$

$$P = V_0 i_0 [\sin^2 \omega t \cos \phi + \frac{\sin 2\omega t \sin \phi}{2}]$$

$$P_{av} = V_0 i_0 [\langle \sin^2 \omega t \rangle \cos \phi + \frac{\langle \sin 2\omega t \rangle \sin \phi}{2}]$$

$$P_{av} = V_0 i_0 [\frac{1}{2} \cos \phi + 0]$$

$$P_{av} = \frac{V_0}{\sqrt{2}} \frac{i_0}{\sqrt{2}} \cos \phi$$

$$\sin 2\theta = 2 \sin \theta \cos \theta$$

$$\sin(A+B) = \sin A \cos B + \cos A \sin B$$

$$P_{av} = \frac{V_o}{\sqrt{2}} \frac{i_o}{\sqrt{2}} \cos \phi$$

$$P_{av} = V_{rms} i_{rms} \cos \phi$$

True Power

Apparent Power

Power factor

$\cos \phi$

$\phi = 0^\circ$

$\phi = 90^\circ$

$$\cos \phi = \frac{R}{Z}$$

$$\cos 0^\circ = \frac{R}{Z}$$

$$I = \frac{R}{Z}$$

$$Z = R$$

Purely resistive  
or  
resonance

$$P_{av} = V_{rms} i_{rms} \cos \phi$$

$$\cos \phi = \frac{R}{Z}$$

$$\cos 90^\circ = \frac{R}{Z}$$

$$0 = \frac{R}{Z}$$

$$R = 0$$

Purely resistive

Purely capacitive  
or  
Purely inductive

# Watt-less current in series LCR circuit



$$V = V_0 \sin \omega t$$

$$i = i_0 \sin(\omega t + \phi)$$


Watt-less  
Current

It is the current

which do not contribute  
in Power of an AC circuit.

$(i \sin \theta \perp V)$

$$P = 0$$

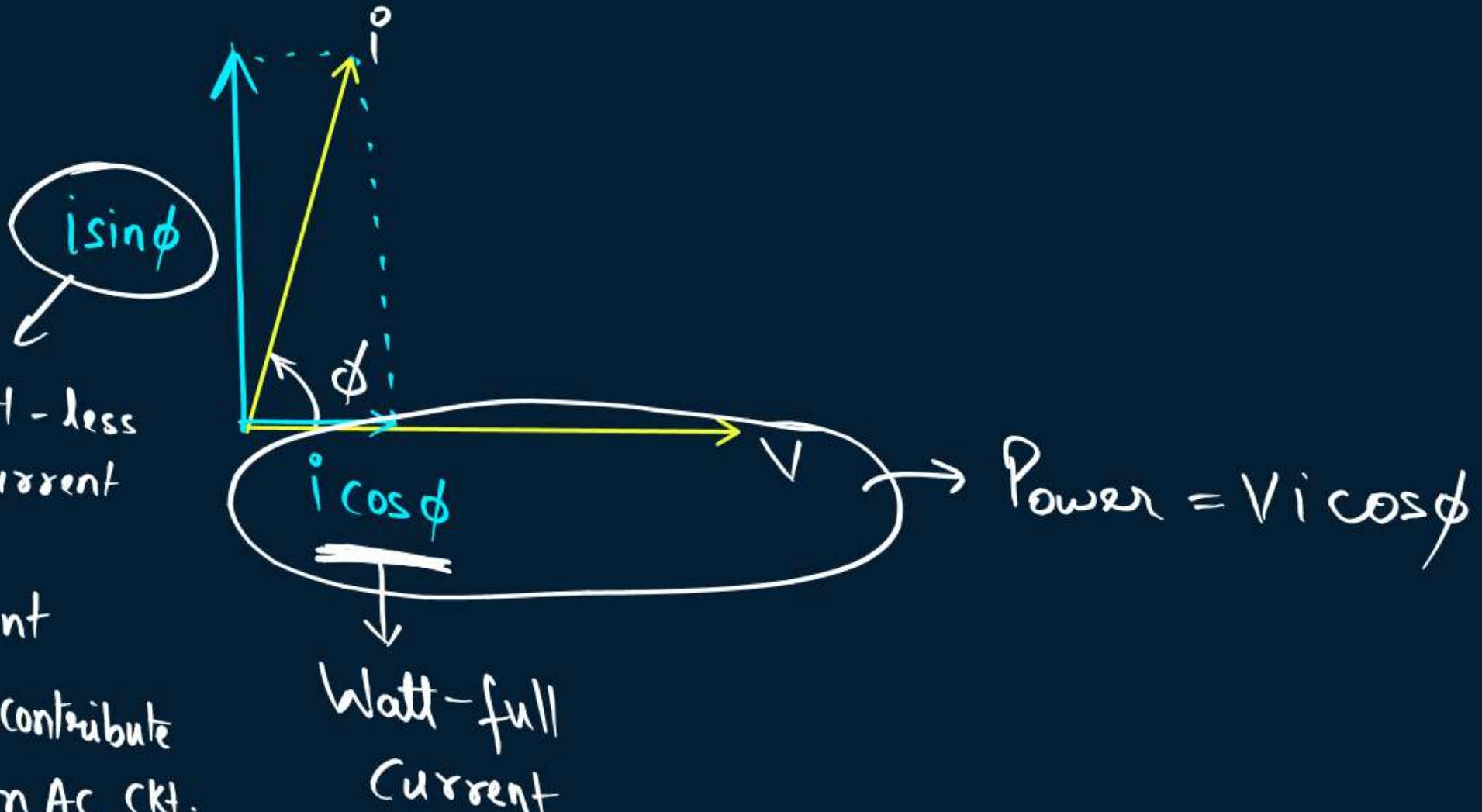



# Resonance in LCR series circuit

↓  
is on LCR ckt.

$$\left\{ \begin{array}{l} X_L = X_C \\ V_L = V_C \end{array} \right\}$$


$$X_L = X_C$$

$$\omega_L = \frac{1}{\omega_C}$$

$$\omega^2 = \frac{1}{LC} \rightarrow$$

resonating Ang. freq.

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

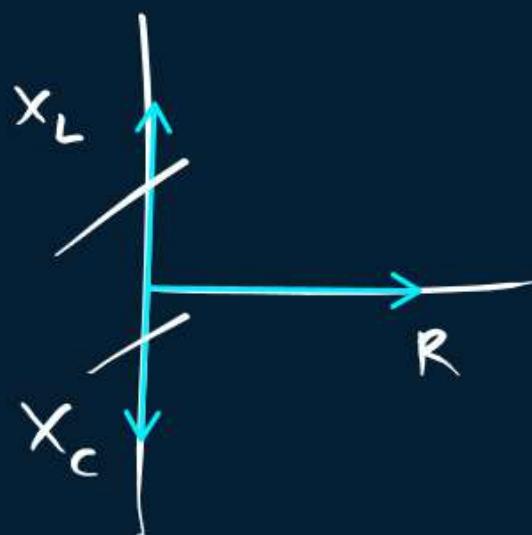

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$2\pi\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$X_L = X_C$$

$$Z = \sqrt{R^2 + (X_C - X_C)^2}$$

$$Z = \sqrt{R^2}$$

resonating frequency

$$Z = R$$

$V_{net} = V_R$




# Homework

Likh Kar Practice x 4  
DPP Try



# PARISHRAM

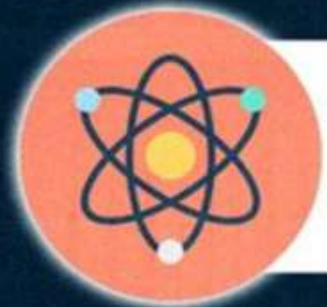


2026

Lecture - 04  
Alternating Currents

PHYSICS


Lecture 04

BY - RAKSHAK SIR

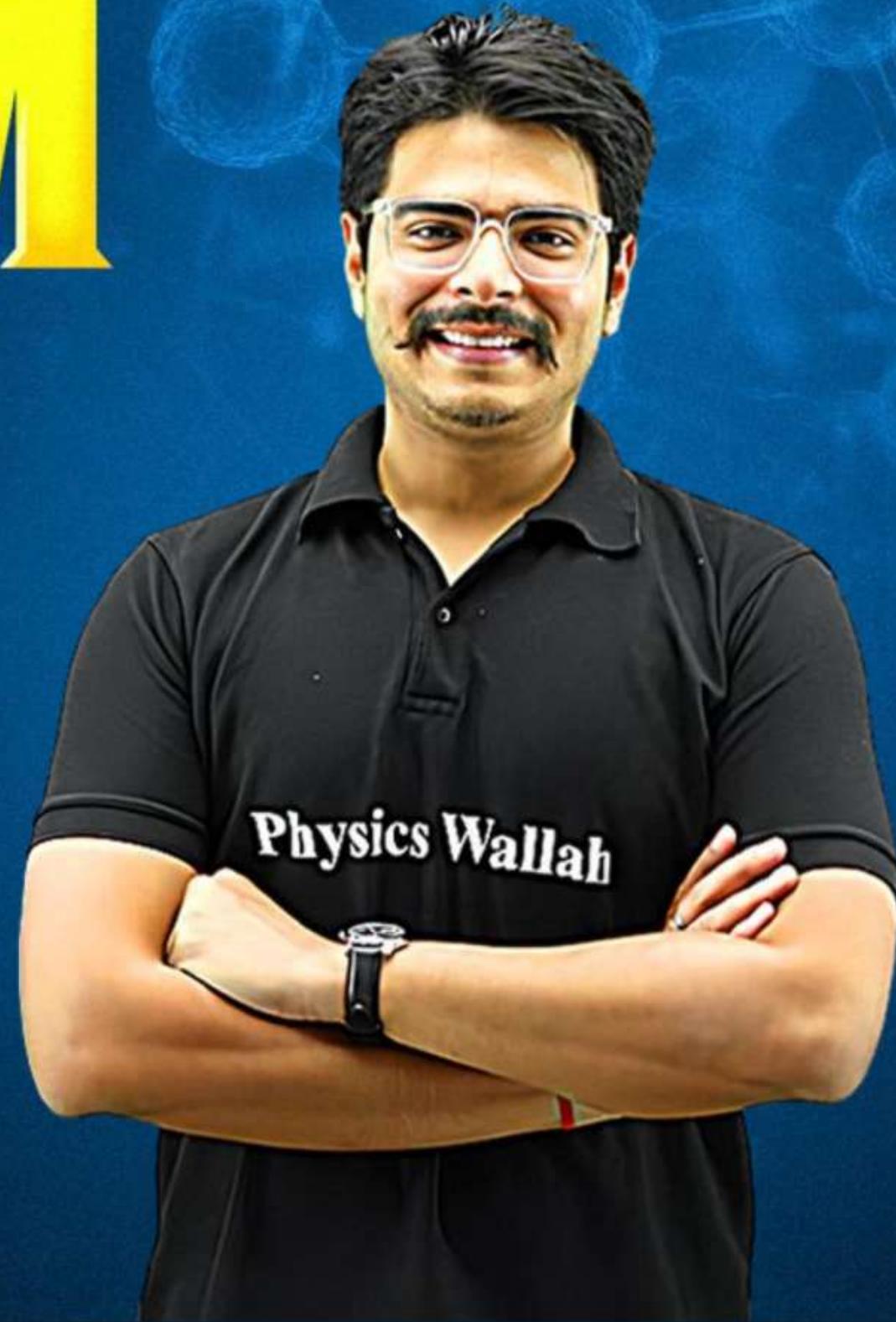
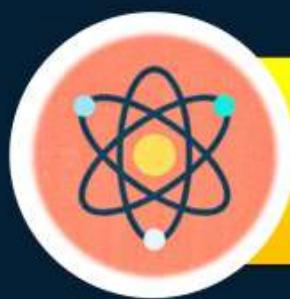
# Topics *to be covered*

- 1 Resonance Contd. ✓
- 2 Transformer ✓
- 3 Practice Questions ✓



# Resonance in LCR series circuit



CKT. Ki frequency  
= Natural frequency

$\downarrow$   
I rise  
 $Z$  low

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{R^2 + (\omega)^2}$$

$$Z = \sqrt{R^2}$$

$$Z = R$$

$$V = iZ$$

$$V = iR$$



To create resonance :-

$$X_L - X_C = 0$$

$$X_L = X_C$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC}$$

resonating  
Ang.  
frequency

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$i \rightarrow$  Amplitude Rise ↑  
Impedance Low ↓

$$V = iZ$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$V = iZ$$

$$\frac{V}{Z} = i \uparrow$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$2\pi f_0 = \frac{1}{\sqrt{LC}}$$

$f_0 = \frac{1}{2\pi\sqrt{LC}}$

*resonating frequency*

$$\text{Power} = V_{\text{rms}} I_{\text{rms}} \cos \phi$$

$$P_{\text{av}} = V_{\text{rms}} I_{\text{rms}} \quad (1)$$

$$P_{\text{av}} = V_{\text{rms}} I_{\text{rms}}$$

$$= \frac{V_0}{\sqrt{2}} \frac{i_0}{\sqrt{2}}$$

$P_{\text{av}} = \frac{V_0 i_0}{2}$

Power factor  
 $\cos \phi = \frac{R}{Z}$

At resonance,

$$Z = R$$


$$\cos \phi = \frac{R}{Z},$$

$$\cos \phi = 1$$

$$\phi = 0^\circ$$



## Example of Radio Tuning

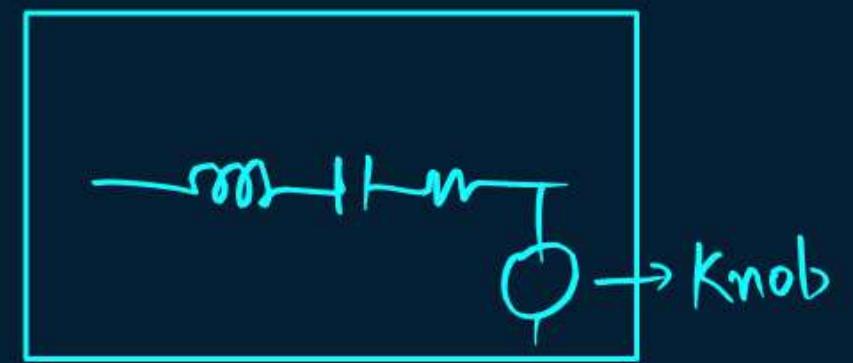

$$X_L = X_C$$




Resonance





$C \rightarrow \text{change}$

$$X_C = \frac{1}{\omega C}$$


# Graph

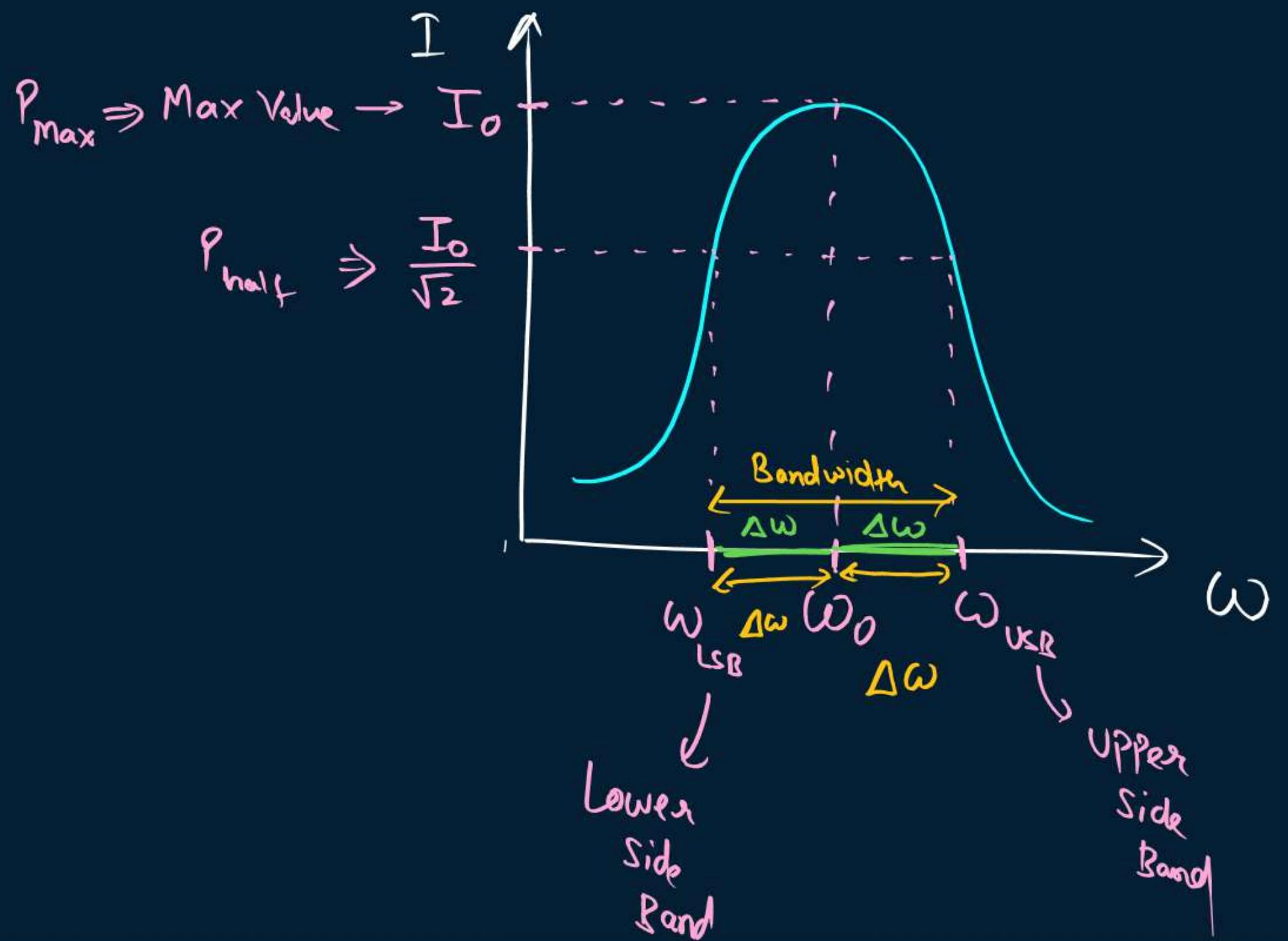

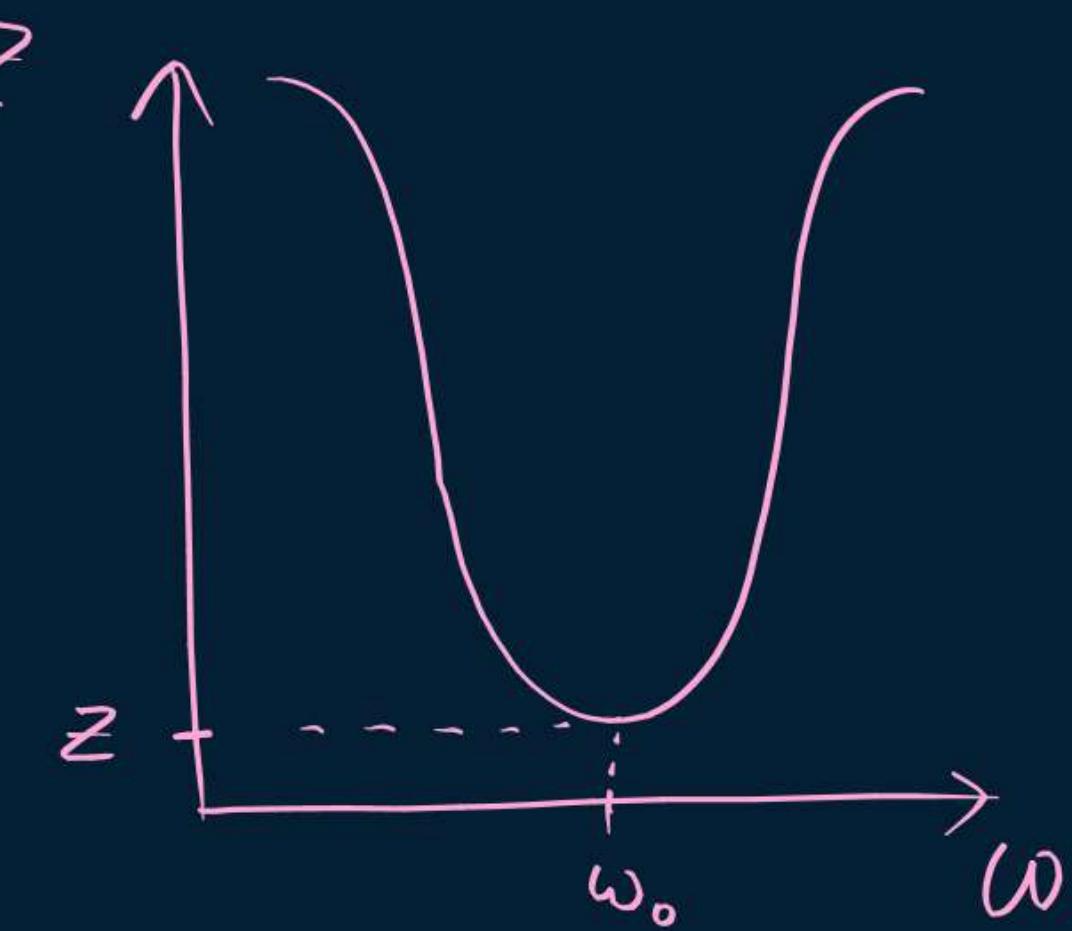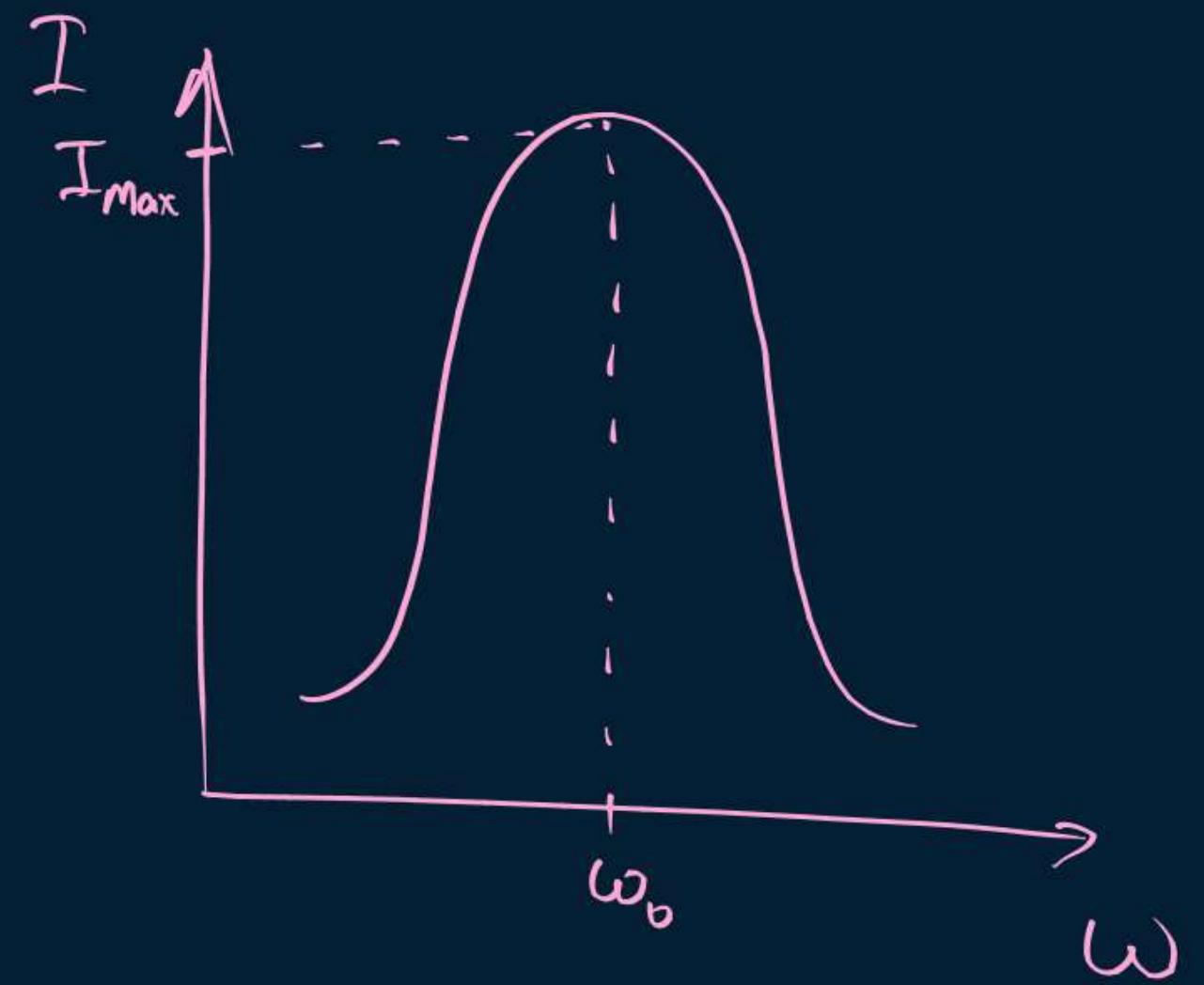



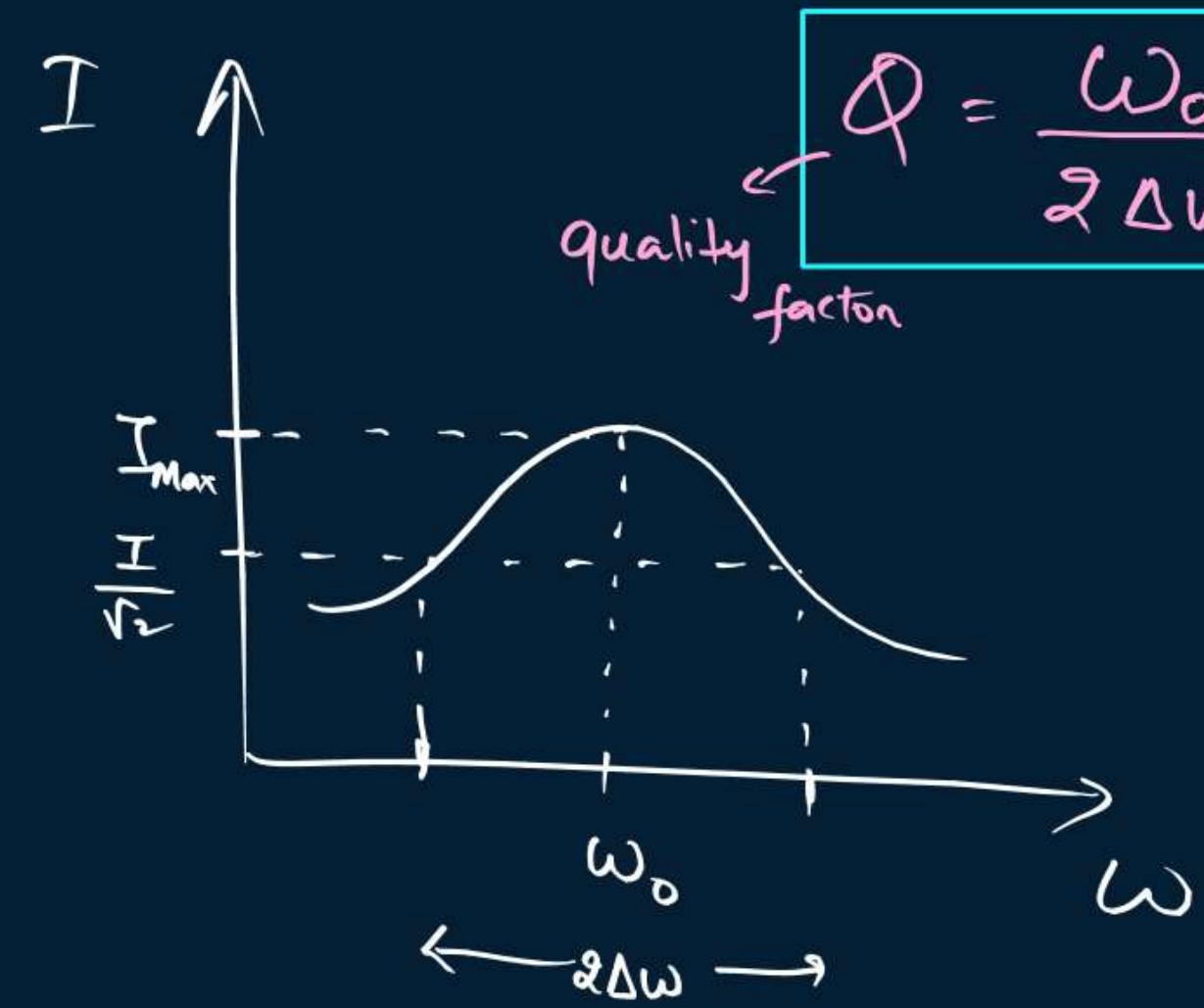
# Quality factor / Sharpness of a Circuit (Q) $\underline{Q\text{-factor}}$



$Q \downarrow$

quality  
factor
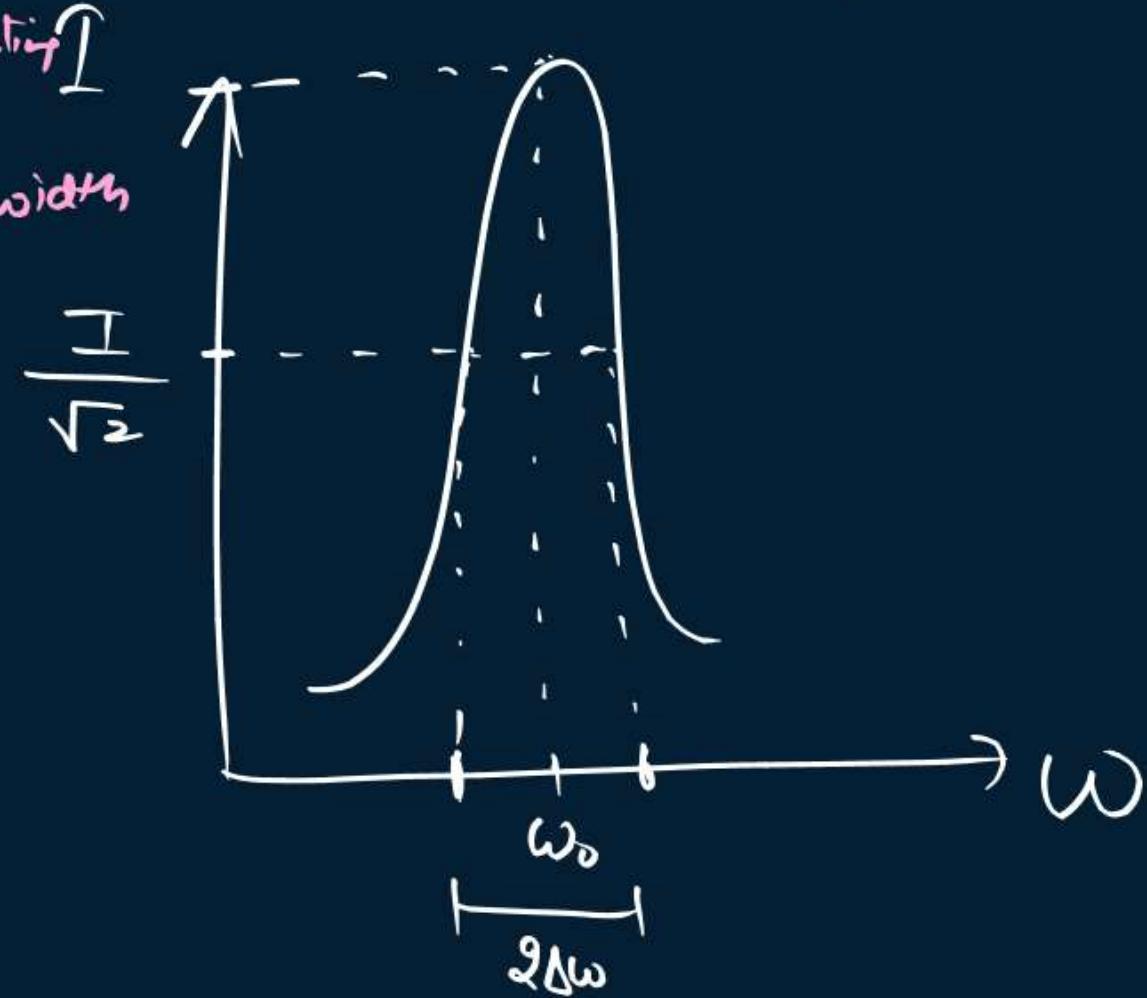
$$Q = \frac{\omega_0}{2\Delta\omega} \rightarrow \begin{array}{l} \text{resonating } I \\ \text{freq} \\ \text{Bandwidth} \end{array}$$



$Q \uparrow$



# Transformer



To step up or step down the voltage.

Principle :- Based on mutual inductance between two coils. Whenever there is change in current in primary coil, there is emf induced in the secondary coil.





# Asli Transformer




OPTIMUS  
PRIME !!!



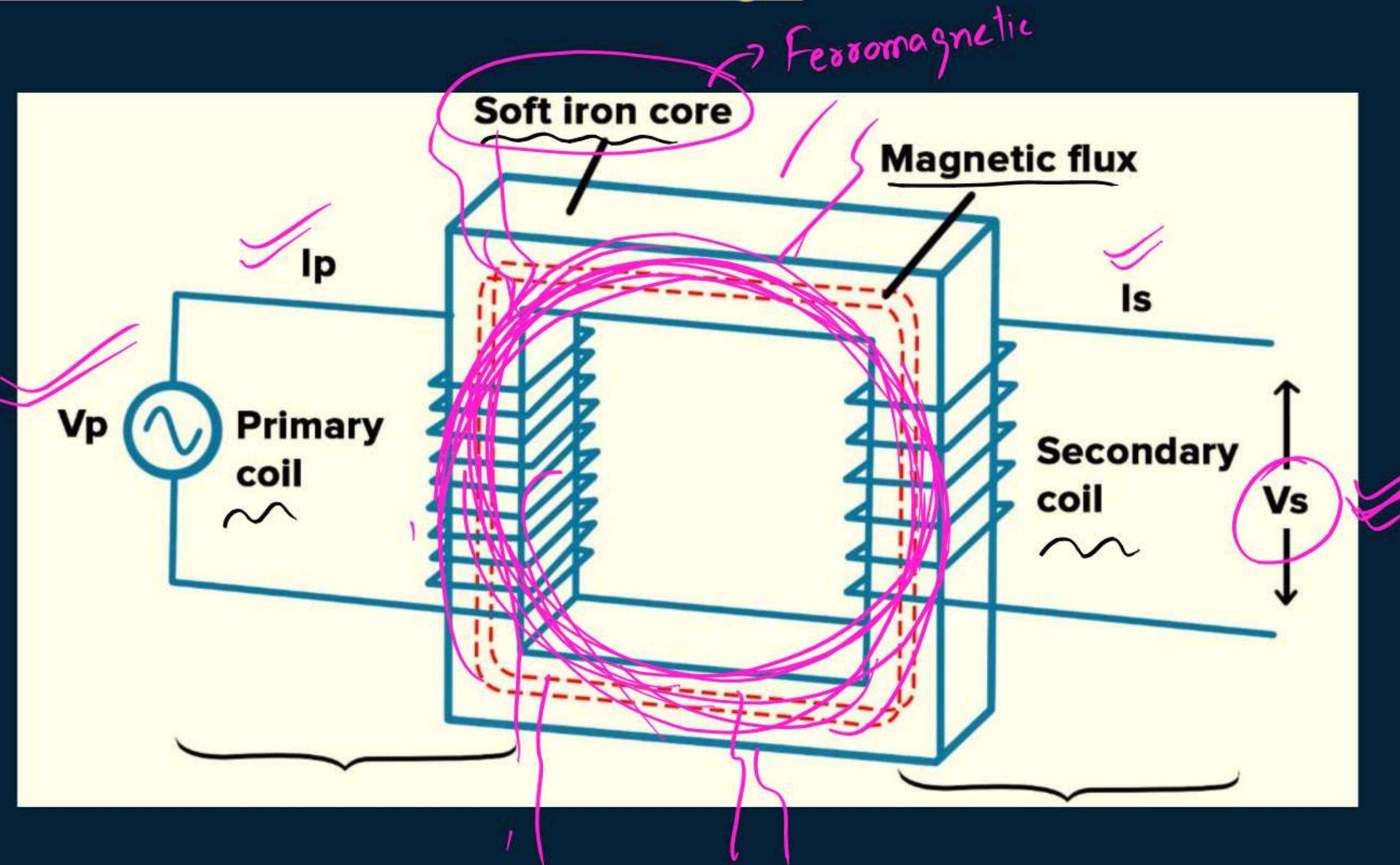
# Construction and Working

$V_p$  - Primary emf  
 $i_p$  - Primary current



$V_s$  - Secondary emf  
 $i_s$  - Secondary current

## a. Step-up Transformer

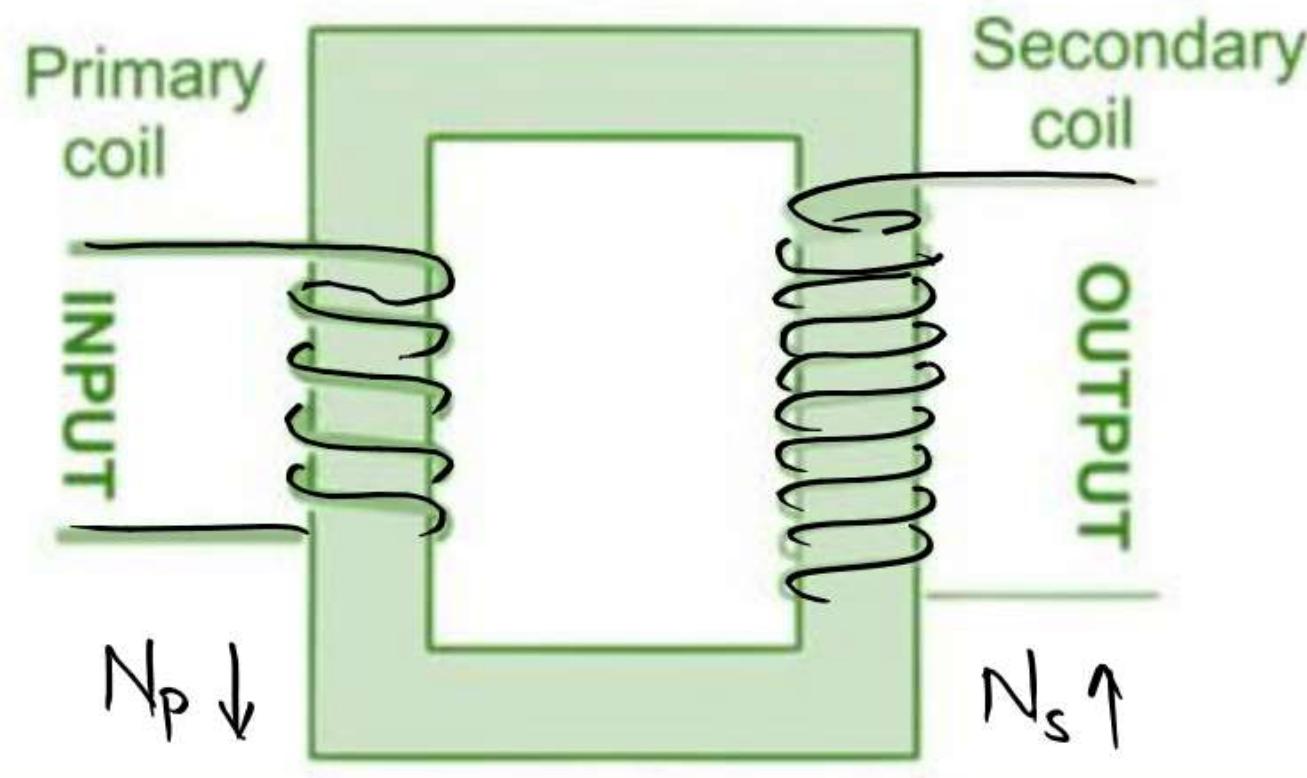

$$\mathcal{E}_p \downarrow$$


$$i_p \uparrow$$

$$\mathcal{E}_q \propto N$$

$$\mathcal{E}_s \uparrow$$

$$i_s \downarrow$$

## b. Step-down Transformer

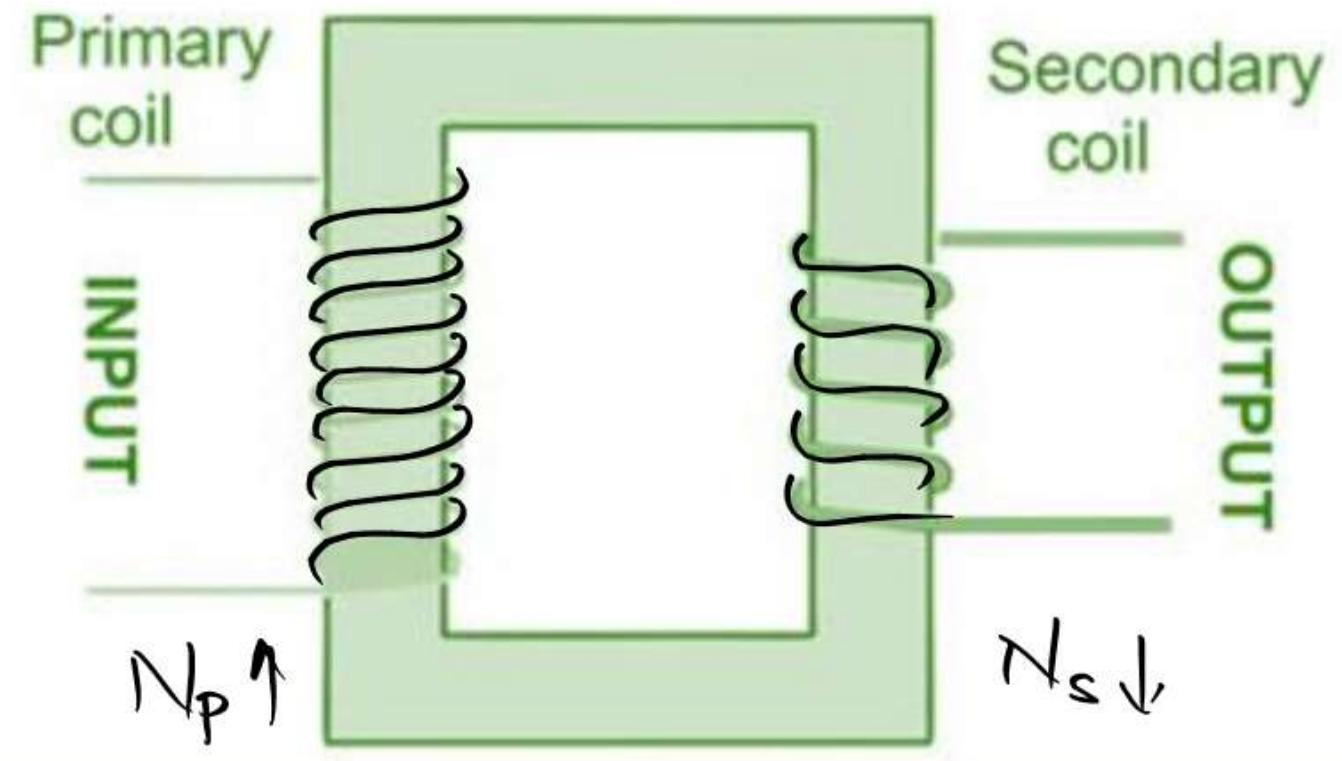

$$\mathcal{E}_p \uparrow$$

$$i_p \downarrow$$

$$\mathcal{E}_s \downarrow$$

$$i_s \uparrow$$



## Ideal Transformer

$$\mathcal{E} \propto N \propto \frac{1}{i}$$

$$P_{\text{input}} = P_{\text{output}}$$

$$\mathcal{E}_P i_P = \mathcal{E}_S i_S$$

Soch ↗

$$\frac{N_P}{N_S} = \frac{\mathcal{E}_P}{\mathcal{E}_S} = \frac{i_S}{i_P}$$

$$\left\{ \mathcal{E} \propto N \propto \frac{1}{i} \right.$$



## Non - Ideal Transformer

$$P_{in} > P_{out}$$

Efficiency of a Transformer

$$\eta = \frac{P_o}{P_i} \times 100$$


Ideal transformer  $\Rightarrow \eta = 100\%$ .



## Losses in Transformer:



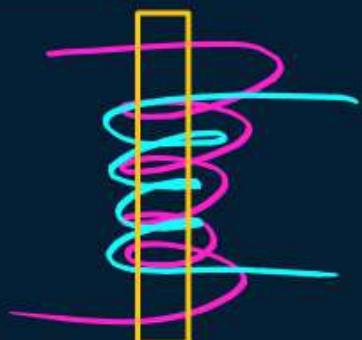1. **Copper Loss:** Due to resistance of the windings, the heat is produced. To reduce it, we use thick wires.  $A \uparrow R \downarrow$
2. **Iron Losses:** Due to eddy currents being produced in the soft iron core, heat is produced. To reduce it we, use laminated core.  $\Rightarrow$  laguer (insulated Material)
3. **Flux Loss:** To reduce it, we mount both coils on a single vertical pole.
4. **Hysteresis Loss:** Due to repeated magnetization and de – magnetization, there will be magnetic fatigue. There will be more energy losses.
5. **Magneto-striction:** Due to humming noise of the transformer.



**QUESTION - 7.1**

A 100 resistor is connected to a 220 V, 50 Hz ac supply.

- (a) What is the rms value of current in the circuit?
- (b) What is the net power consumed over a full cycle?



$$\begin{aligned}
 P_{av} &= V_{rms} I_{rms} \cos \phi \\
 &= V_{rms} I_{rms} \\
 &= 220 \times 2.2 \\
 &= 484 \text{ W}
 \end{aligned}$$

$$V_{rms} = 220V$$

$$I_{rms} = ?$$

$$V_{rms} = I_{rms} R$$

$$220 = I_{rms} \times 100$$

$$I_{rms} = \frac{220}{100} = 2.2A$$

## QUESTION - 7.2

(a) The peak voltage of an ac supply is 300 V. What is the rms voltage?

(b) The rms value of current in an ac circuit is 10 A. What is the peak current?

$$b) I_{\text{rms}} = 10 \text{ A}$$

$$I_0 = ?$$

$$I_{\text{rms}} = \frac{I_0}{\sqrt{2}}$$

$$I_0 = \frac{I_{\text{rms}}}{\sqrt{2}}$$

$$I_0 = 1.414 \times 10 = 14.14 \text{ A}$$

$$a) V_o = 300 \text{ V}$$

$$V_{\text{rms}} = \frac{V_o}{\sqrt{2}} = \frac{300}{\sqrt{2}} \text{ V}$$

**QUESTION - 7.3**

A 44 mH inductor is connected to 220 V, 50 Hz ac supply. Determine the rms value of the current in the circuit.

$$L = 44 \times 10^{-3} \text{ H}$$

$$V_{\text{rms}} = 220 \text{ V}$$

$$\nu = 50 \text{ Hz}$$

$$I_{\text{rms}} = ?$$

$$V = I R$$

$$V_{\text{rms}} = I_{\text{rms}} X_L$$

$$V_{\text{rms}} = I_{\text{rms}} \omega L$$

$$V_{\text{rms}} = I_{\text{rms}} 2\pi\nu L$$

$$220 = I_{\text{rms}} \times 2 \times 3.14 \times 50 \times 44 \times 10^{-3}$$

## QUESTION - 7.4



A 60  $\mu\text{F}$  capacitor is connected to a 110 V, 60 Hz ac supply. Determine the rms value of the current in the circuit.

$$C = 60 \mu\text{F} = 60 \times 10^{-6} \text{ F}$$

$$V_{\text{rms}} = 110 \text{ V}$$

$$\nu = 60 \text{ Hz}$$

$$I_{\text{rms}} = ?$$

$$V = IR$$

$$V_{\text{rms}} = I_{\text{rms}} X_c$$

$$V_{\text{rms}} = I_{\text{rms}} \frac{1}{\omega C}$$

$$V_{\text{rms}} = I_{\text{rms}} \frac{1}{2\pi\nu C}$$

$$V_{\text{rms}} 2\pi\nu C = I_{\text{rms}}$$

$$110 \times 2 \times 3.14 \times 60 \times 60 \times 10^{-6} = I_{\text{rms}}$$

**QUESTION - 7.5**

In Exercises 7.3 and 7.4, what is the net power absorbed by each circuit over a complete cycle. Explain your answer.

7.3  $\rightarrow$  <sup>Pure</sup> Inductive ( $\phi = 90^\circ$ )

7.4  $\rightarrow$  <sup>Pure</sup> Capacitive ( $\phi = 90^\circ$ )

$$P_{av} = V_{rms} i_{rms} \cos\phi$$

$$= V_{rms} i_{rms} \cos(90^\circ)$$

$$P_{av} = 0$$

## QUESTION - 7.6

A charged  $30 \mu\text{F}$  capacitor is connected to a  $27 \text{ mH}$  inductor. What is the angular frequency of free oscillations of the circuit?

$$\omega = ?$$

$$C = 30 \mu\text{F} = 30 \times 10^{-6} \text{ F}$$

$$L = 27 \text{ mH} = 27 \times 10^{-3} \text{ H}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

↙ الفع | sec

## QUESTION - 7.7

A series LCR circuit with  $R = 20 \text{ Ohm}$ ,  $L = 1.5 \text{ H}$  and  $C = 35 \mu\text{F}$  is connected to a variable-frequency  $200 \text{ V ac supply}$ .

When the frequency of the supply equals the natural frequency of the circuit, what is the average power transferred to the circuit in one complete cycle?

$$V_{\text{rms}} = 200 \text{ V}$$

$$i_{\text{rms}} = ?$$

$$V_{\text{rms}} = i_{\text{rms}} Z$$

$$V_{\text{rms}} = i_{\text{rms}} R$$

$$\frac{200}{10} = i_{\text{rms}} \times 20$$

$$i_{\text{rms}} = 10 \text{ A}$$

resonance ( $Z = R$ )

$$\begin{aligned} P_{\text{av}} &= V_{\text{rms}} i_{\text{rms}} \cos \phi \\ &= V_{\text{rms}} i_{\text{rms}} \\ &= 200 \times 10 \\ &= 2000 \text{ Watt} \end{aligned}$$

## QUESTION - 7.8

A series LCR circuit connected to a variable frequency  $230\text{ V}$  source.

~~$L = 5.0\text{ H}, C = 80\mu\text{F}, R = 40\text{ Ohm.}$~~

- (a) Determine the source frequency which drives the circuit in resonance.
- (b) Obtain the impedance of the circuit and the amplitude of current at the resonating frequency.
- (c) Determine the rms potential drops across the three elements of the circuit. Show that the potential drop across the LC combination is zero at the resonating frequency.

$$a) \omega_0 = \frac{1}{\sqrt{LC}}$$

$\text{rad/sec}$

$$b) \text{At resonance}$$


$$Z = R$$

$$Z = \omega_0 L$$

$$i_{\text{rms}} = \frac{i_0}{\sqrt{2}}$$

$$i_0 = \sqrt{2} i_{\text{rms}}$$
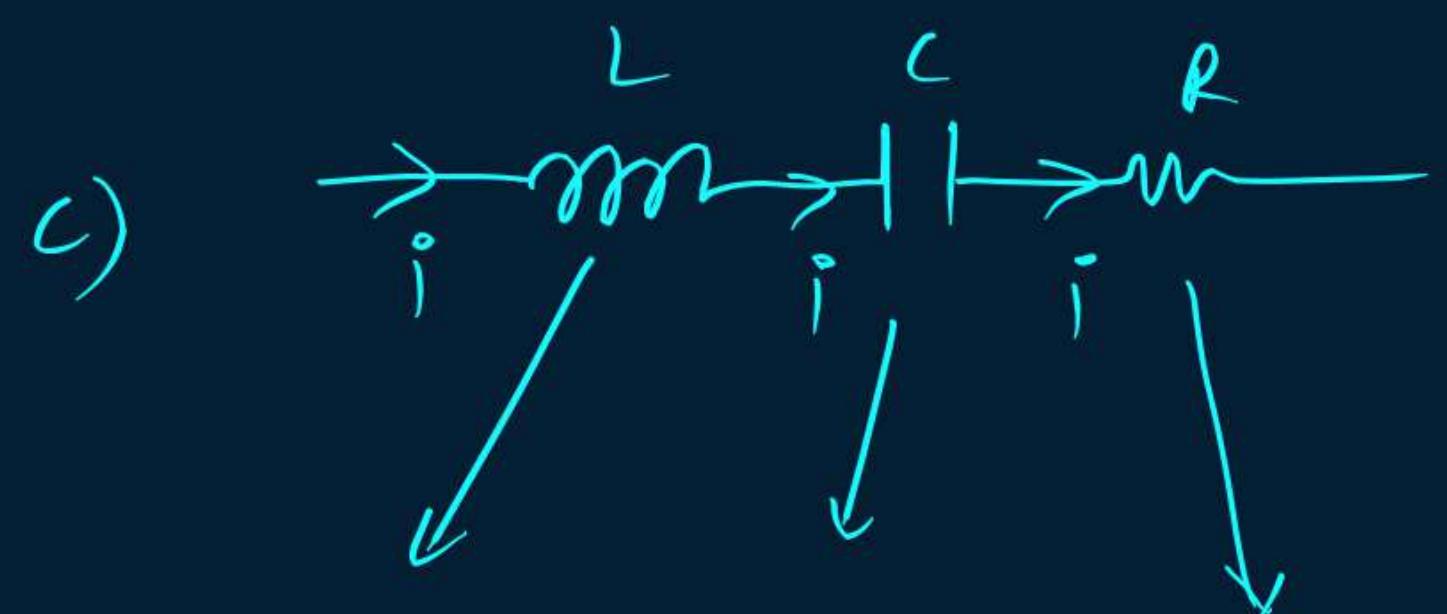
$$\begin{aligned} V_{\text{rms}} &= I_{\text{rms}} Z \\ 230 &= I_{\text{rms}} R \end{aligned}$$



$$\begin{aligned}
 V_L &= I X_L & V_C &= I X_C & V_R &= I R \\
 &= I_{\text{rms}} \omega L & & = \frac{I_{\text{rms}}}{\omega C} & & = I_{\text{rms}} R
 \end{aligned}$$



# Homework

Was it a ~~CBS~~ 10 Ques

Confidence Booster

session

Notes x 4 Baar Pakka Homiie

Solved Examples of NCERT